


Test pulse circuit for amplifier of charged particle detector in KOTO experiment

Outline

- KOTO experiment
- UCV for KOTO
- UCV Amplifier
- Test pulse circuit (TP)
- Design
- Operation check
- Conclusion



KOTO experiment

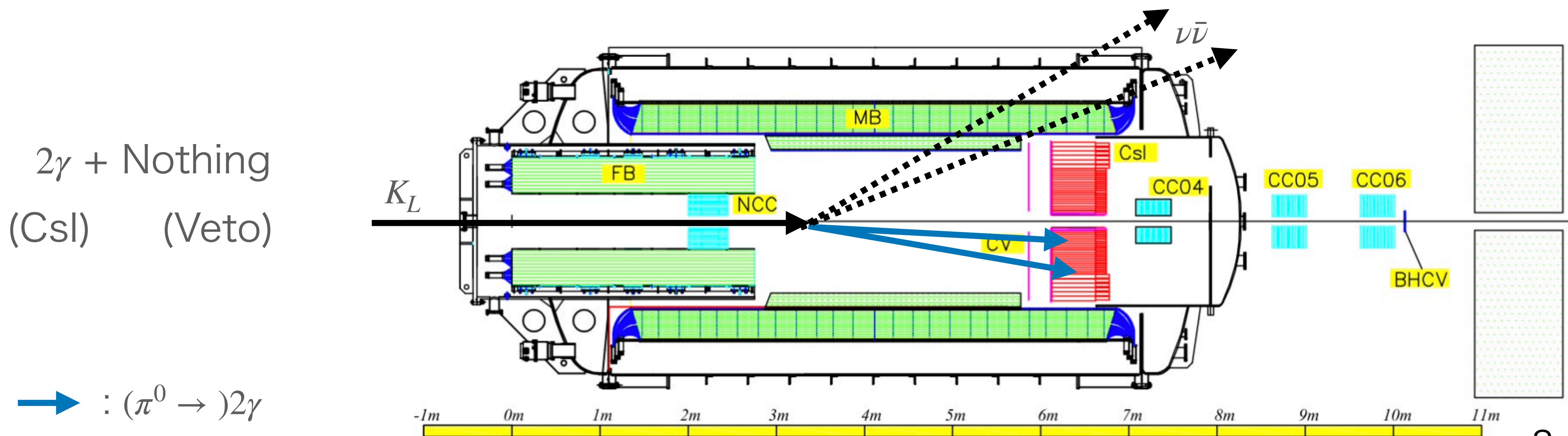- KOTO: search for the CP violating decay $K_L \rightarrow \pi^0 \nu \bar{\nu}$
- $BR(K_L \rightarrow \pi^0 \nu \bar{\nu})_{SM} = 3 \times 10^{-11}$
- Small theoretical uncertainty (~2%) -> easy to find the effect of New Physics



Upstream Charged Veto(UCV) for KOTO

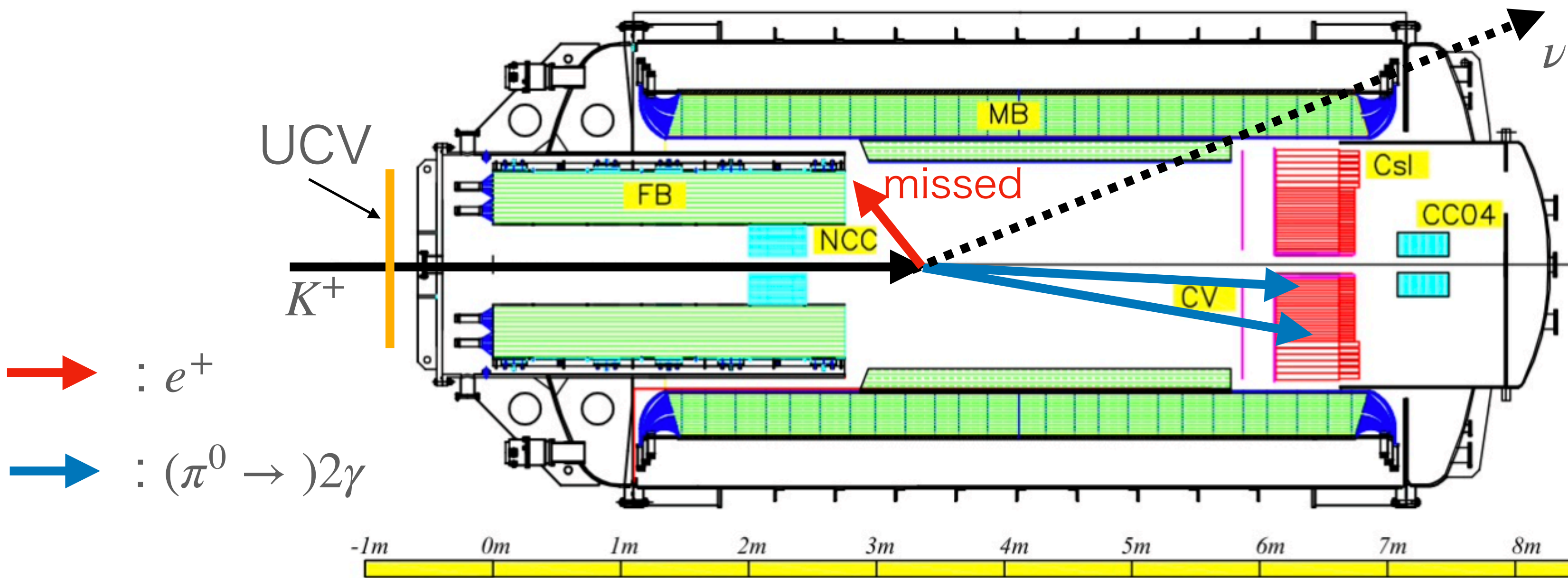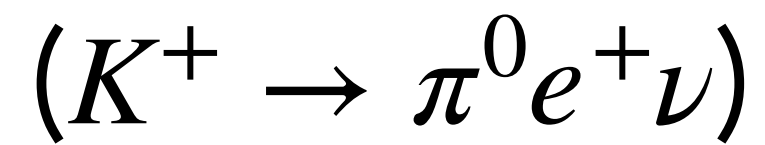- Small K^+ contamination in K_L beam is a source of a major background




→ : e^+
→ : $(\pi^0 \rightarrow)2\gamma$

Ref: <https://koto.kek.jp/exp/detector/index.html>



UCV
PMT (7 × 2)


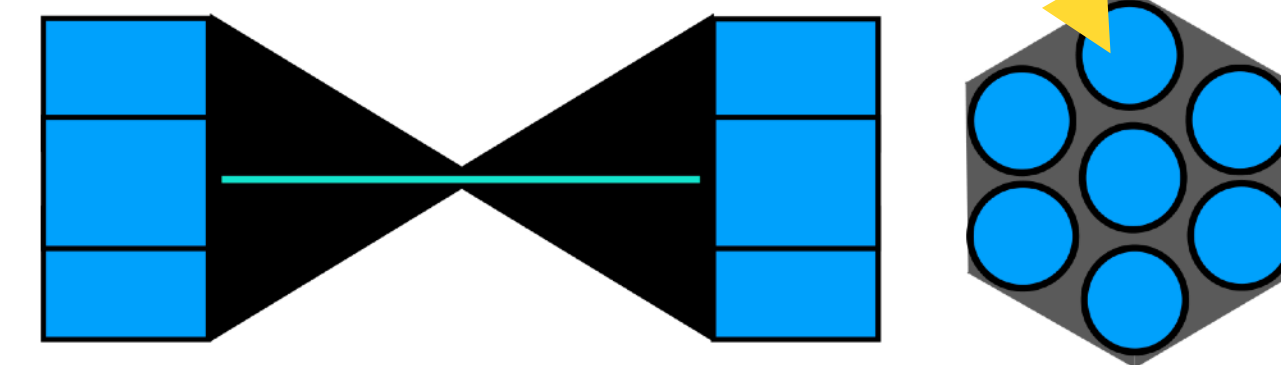


- To veto K^+ , we are developing charged particle detector (UCV)

UCV Amplifier

Roles

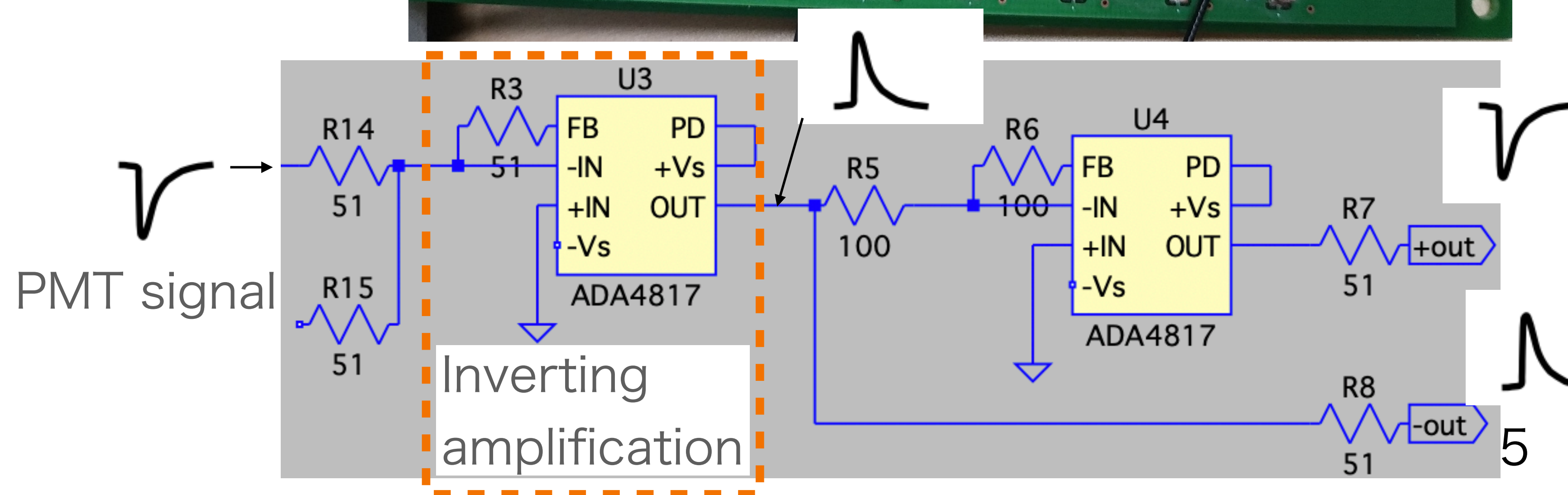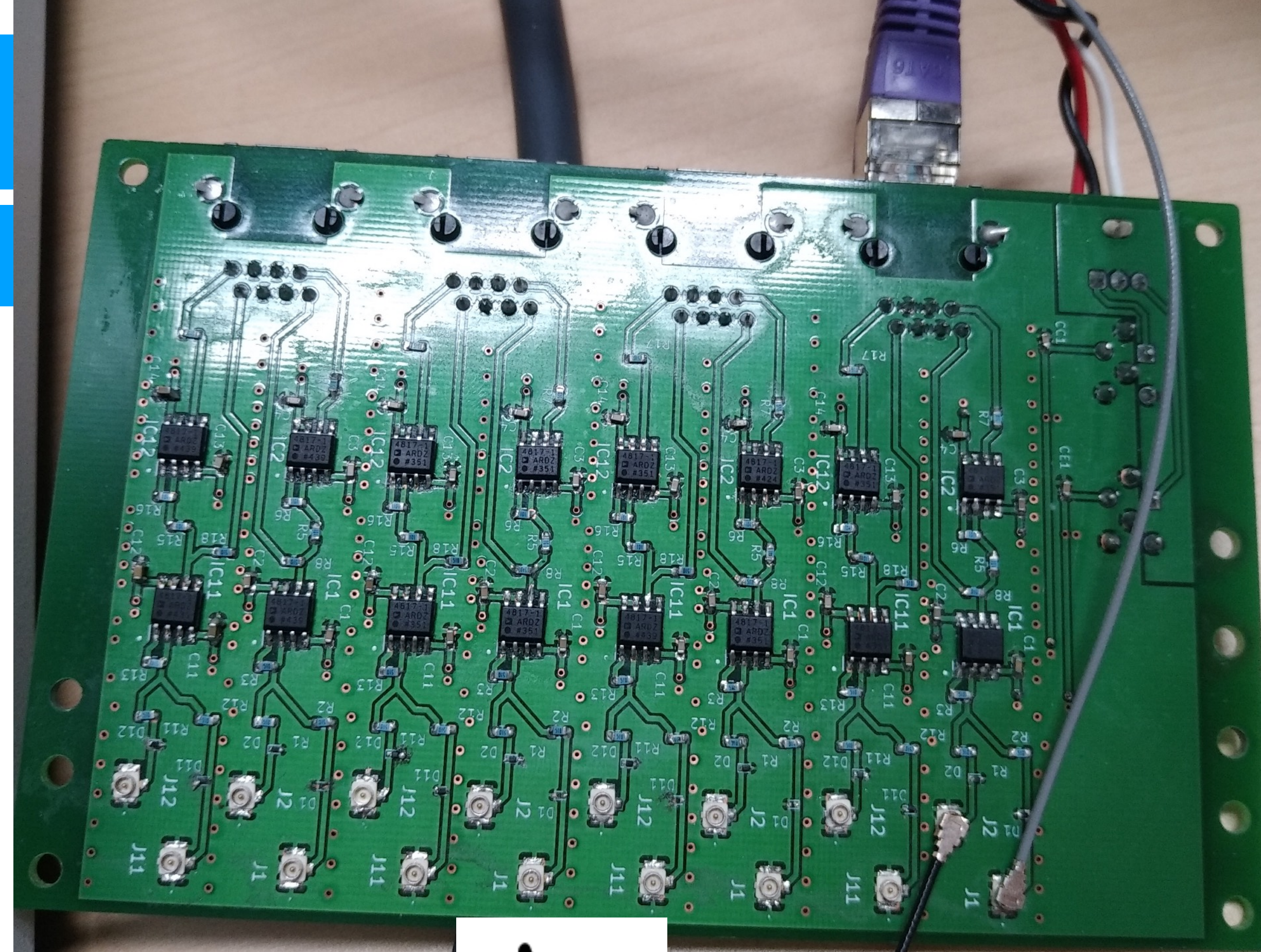
- Sum up two PMT channels (14 PMT outputs -> 7 ADC channels)
- Differential output to cancel common-mode noise picked up in the signal transmission
- Gain : 1



Test Pulse (TP) circuit

Roles

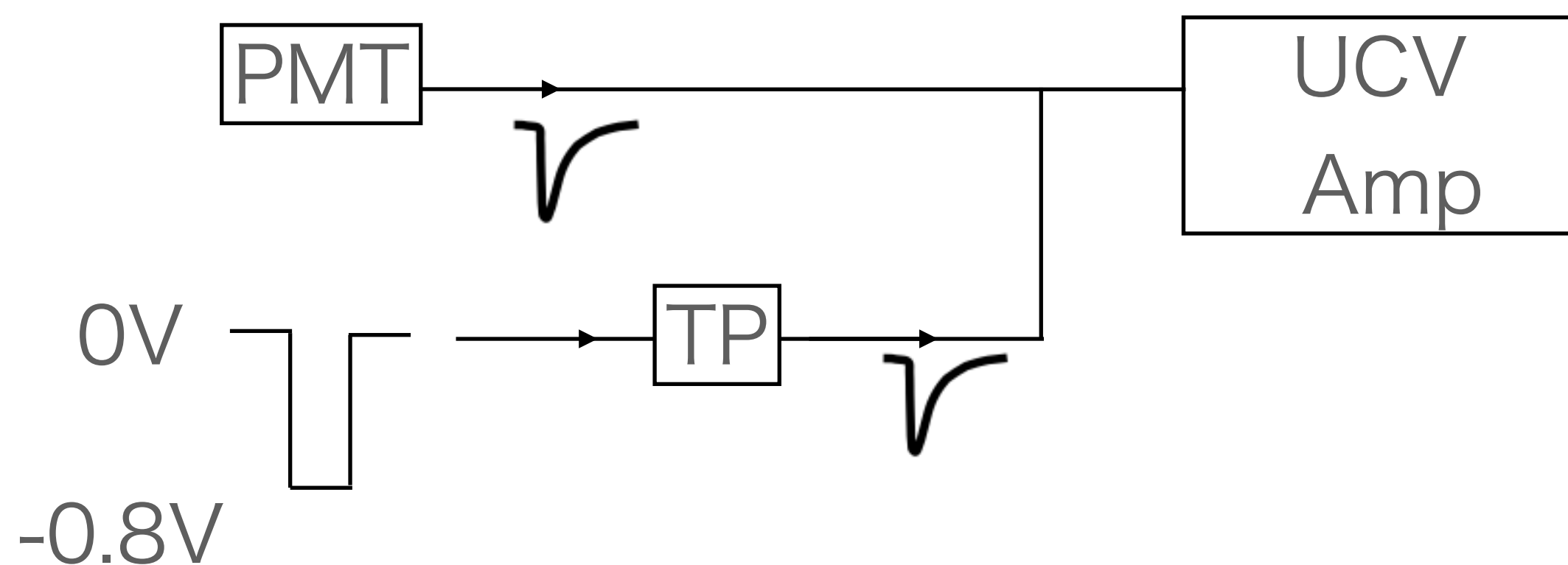- Amplifies the signal, shapes it into a PMT-like waveform, and sends it to the UCV amplifier
 - To check that the UCV amplifiers are working
 - To check the timing variations between amplifier channels



	Current	Voltage(50Ω)
1 (Yes)	-16mA	-0.8V
0 (No)	0mA	0V


NIM standard

Test Pulse (TP) circuit

Motivation of my study




I did two checks to meet the demands for the TP circuit

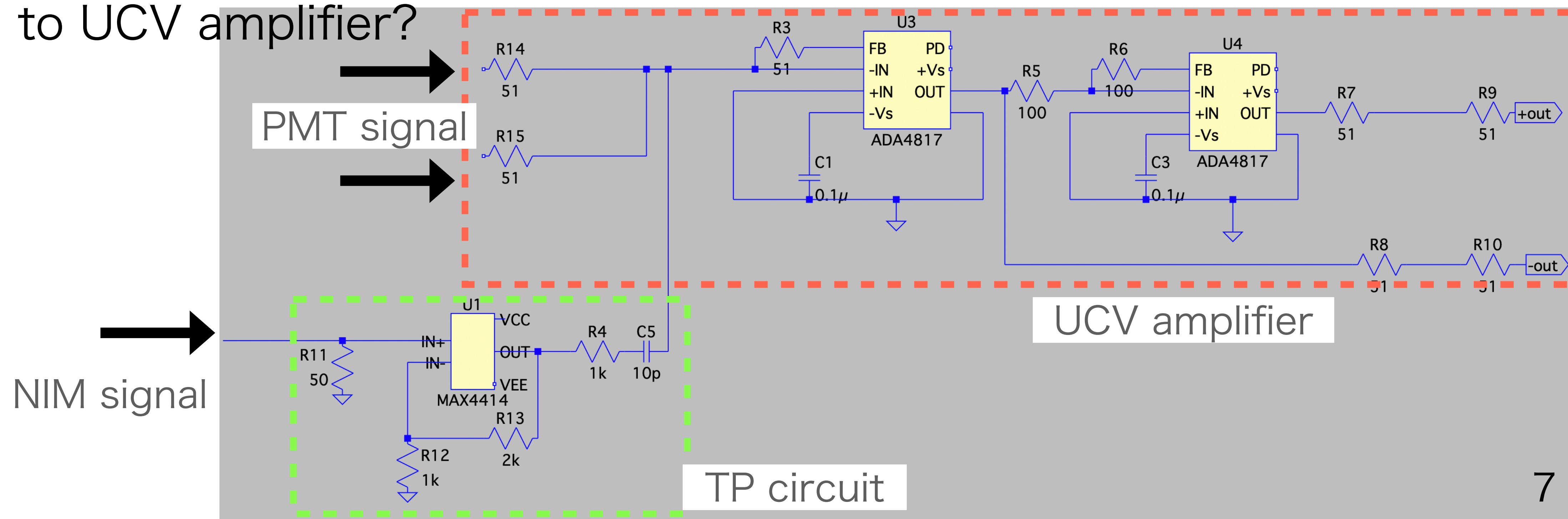- Check 1: Can we see test signal from TP at Amplifier output?
- Check 2: Is there any effect on signal from PMT when we add TPI to UCV amplifier?





Design

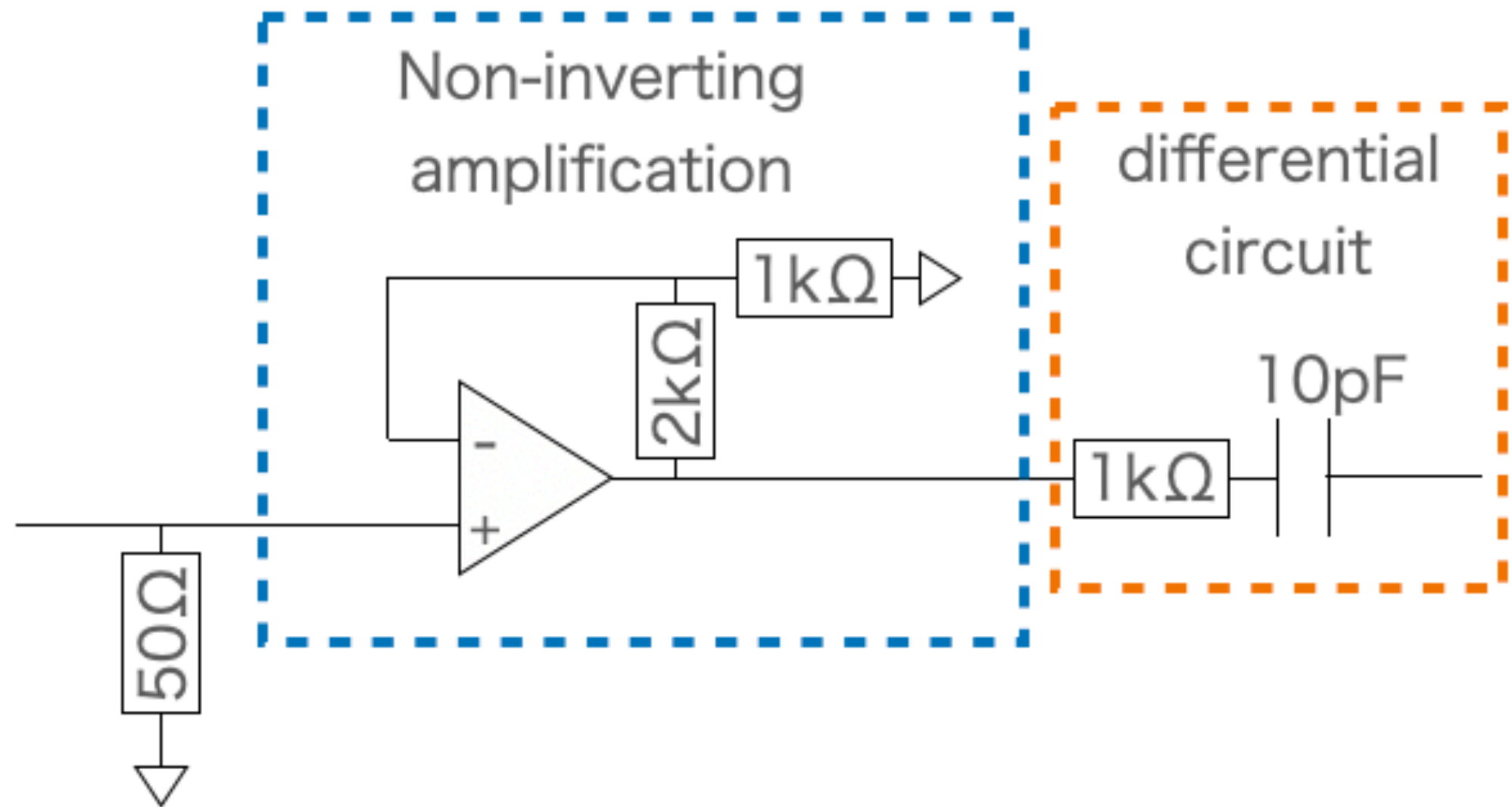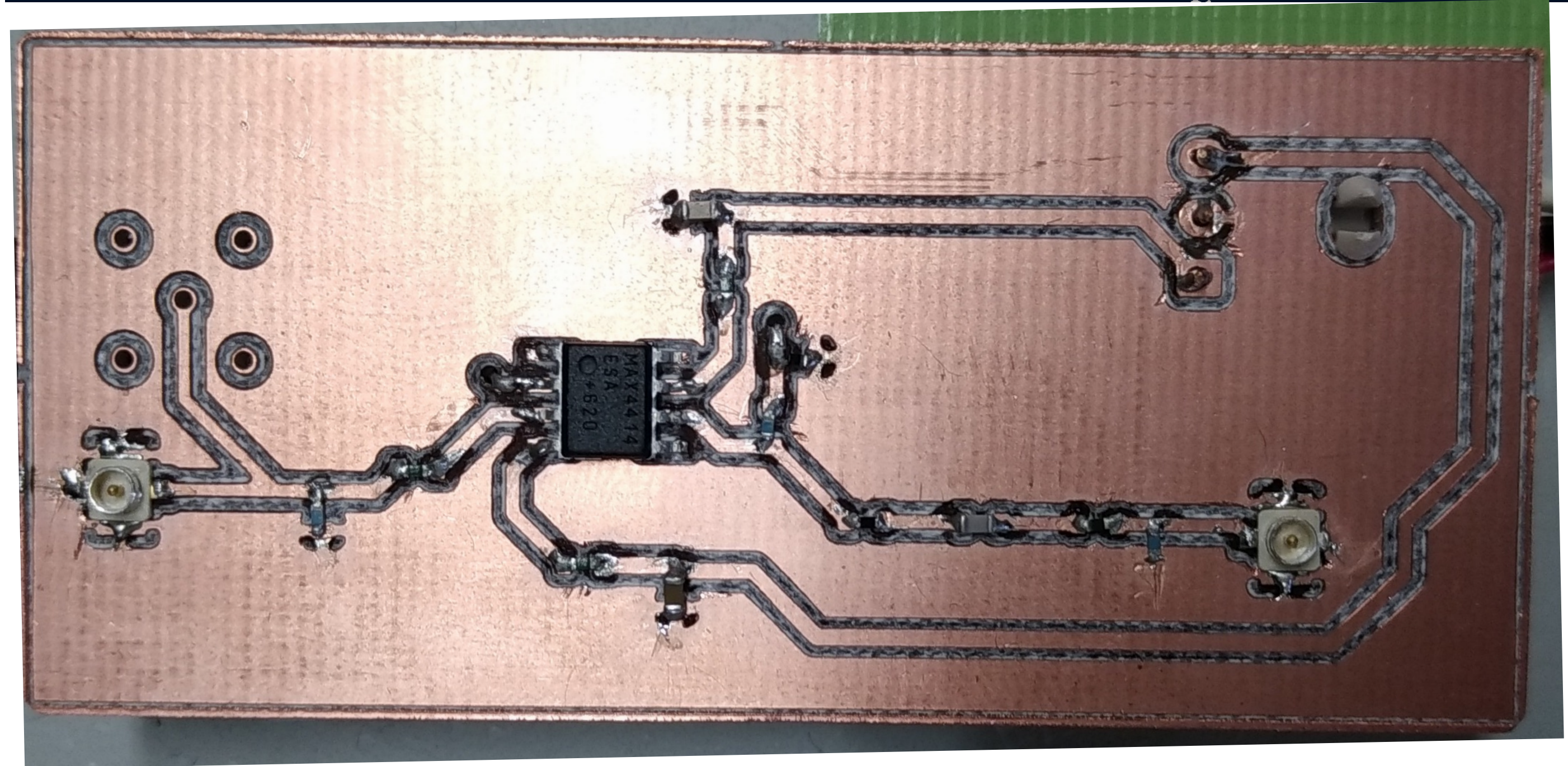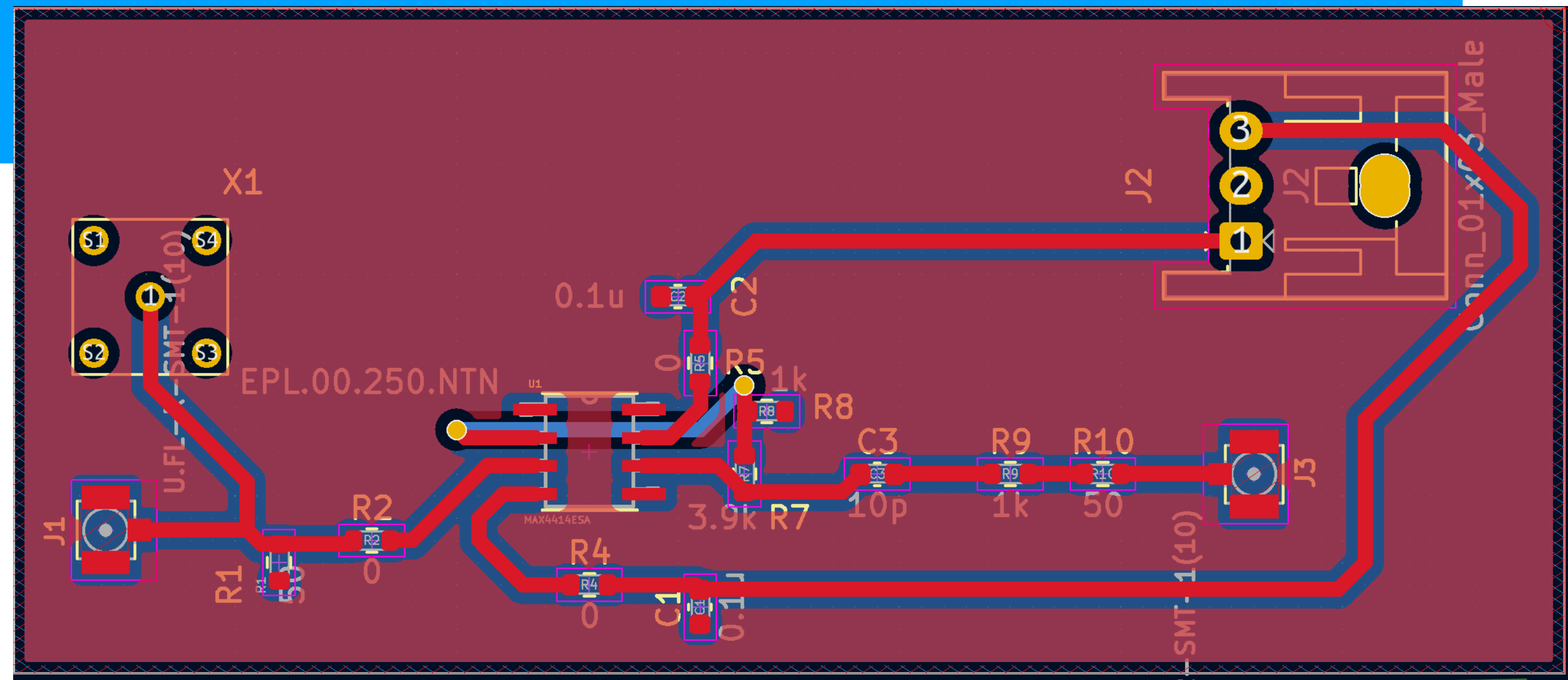- Used KiCad, and made the circuit board pattern




Operation check

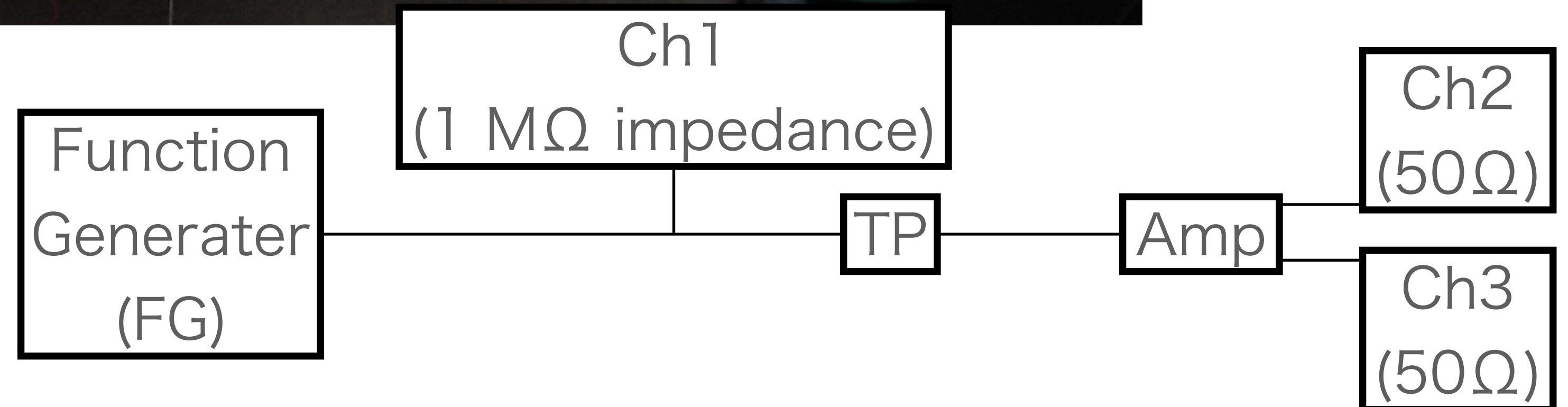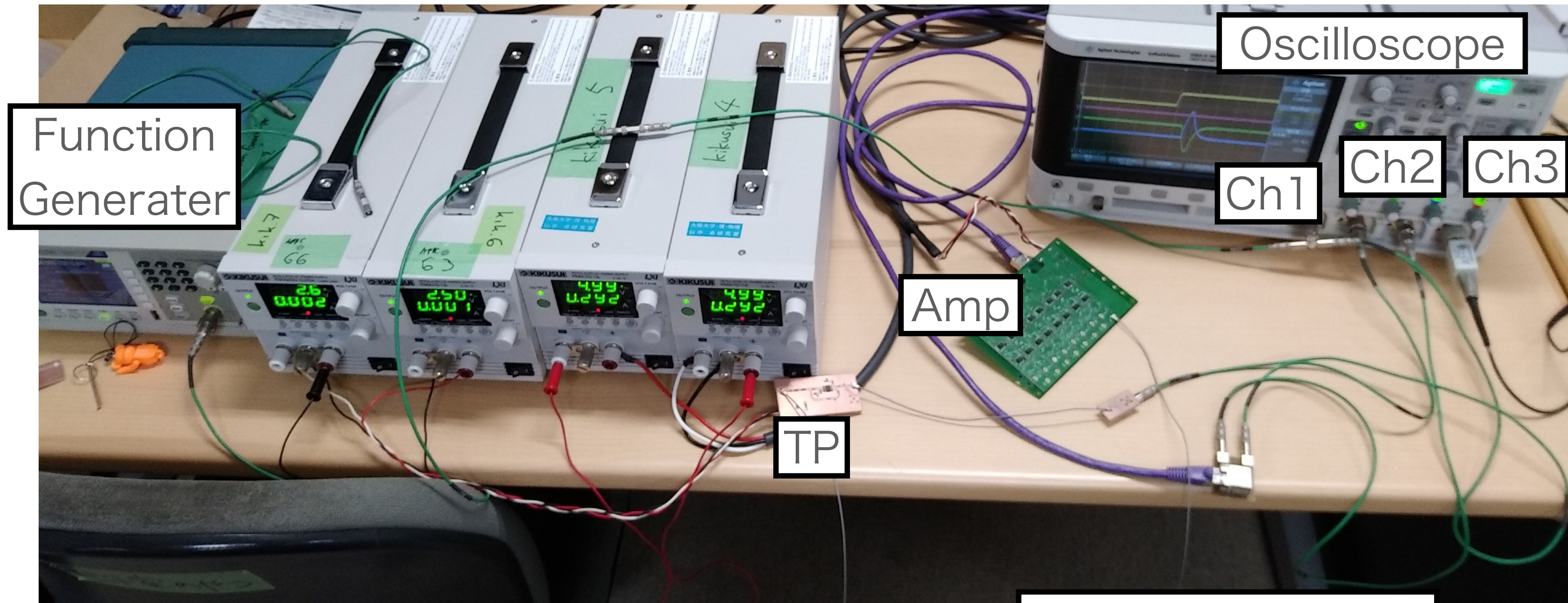Set up of check 1: Can we see test signal from TP at Amplifier output?




Operation check

Output waveform

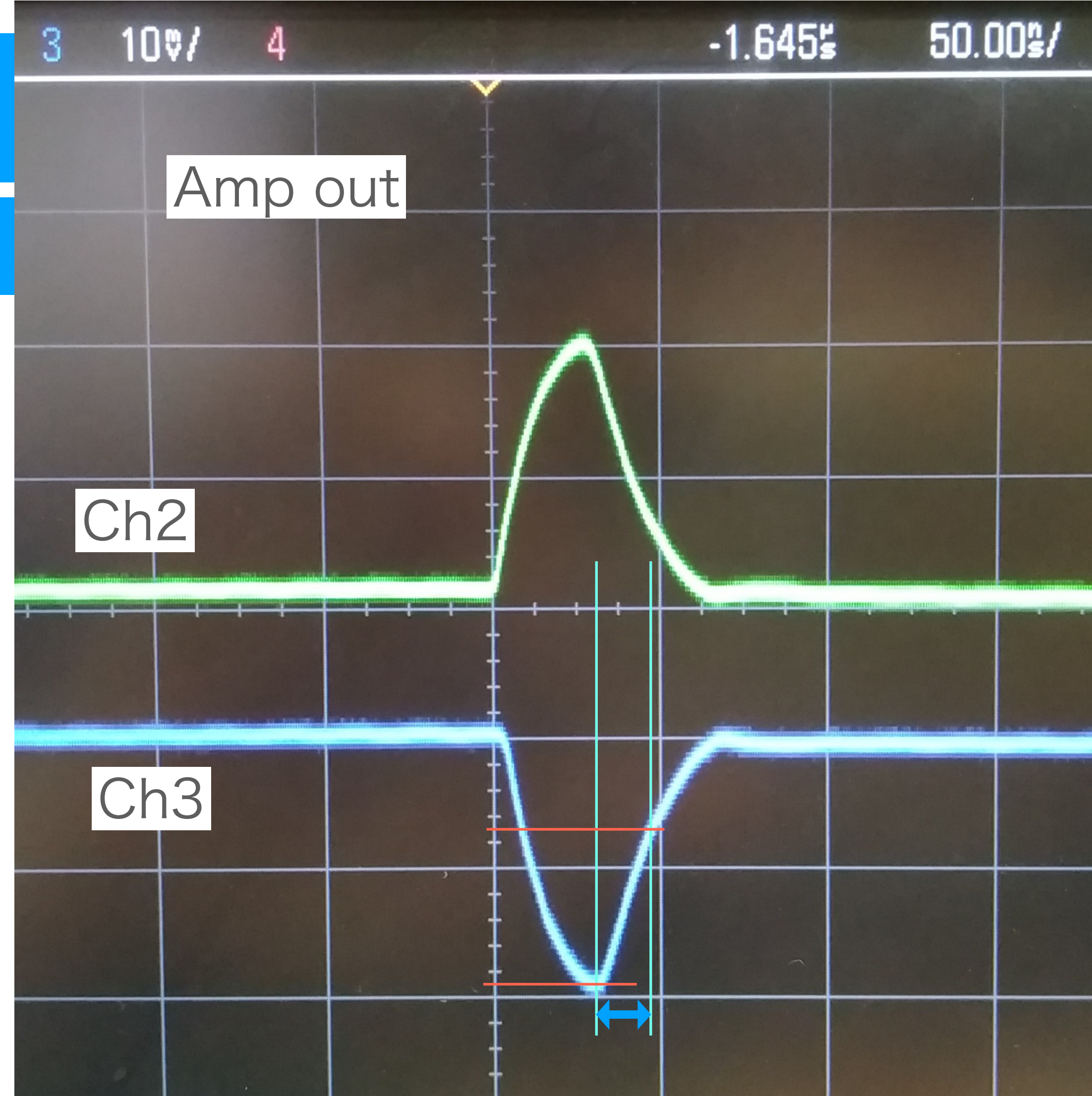


Calculated time constant : $1k\Omega \times 10pF = 10ns$

Measured time : 15 ns

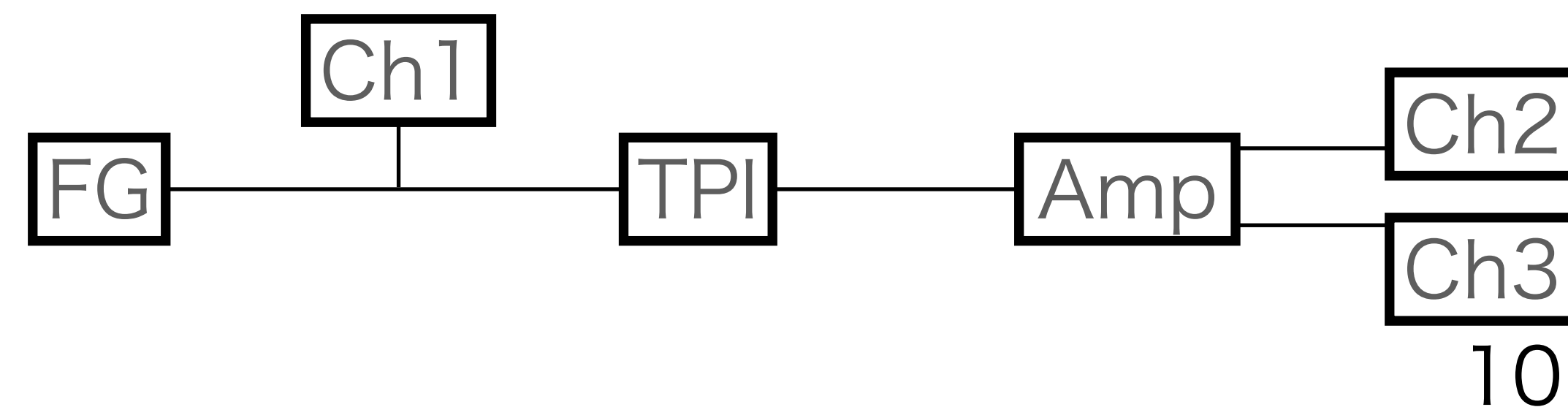


Operation check


Effect on main signal

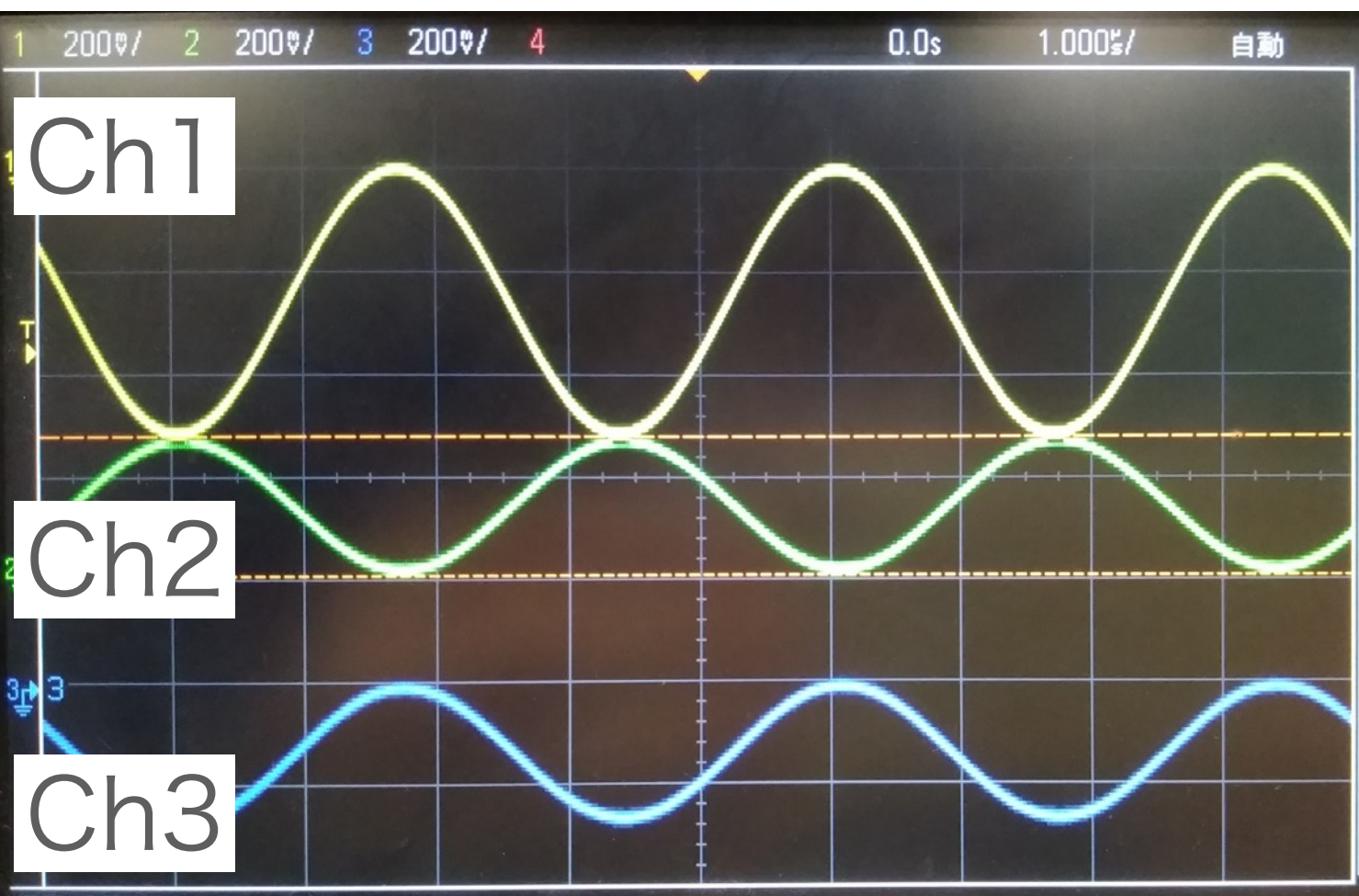

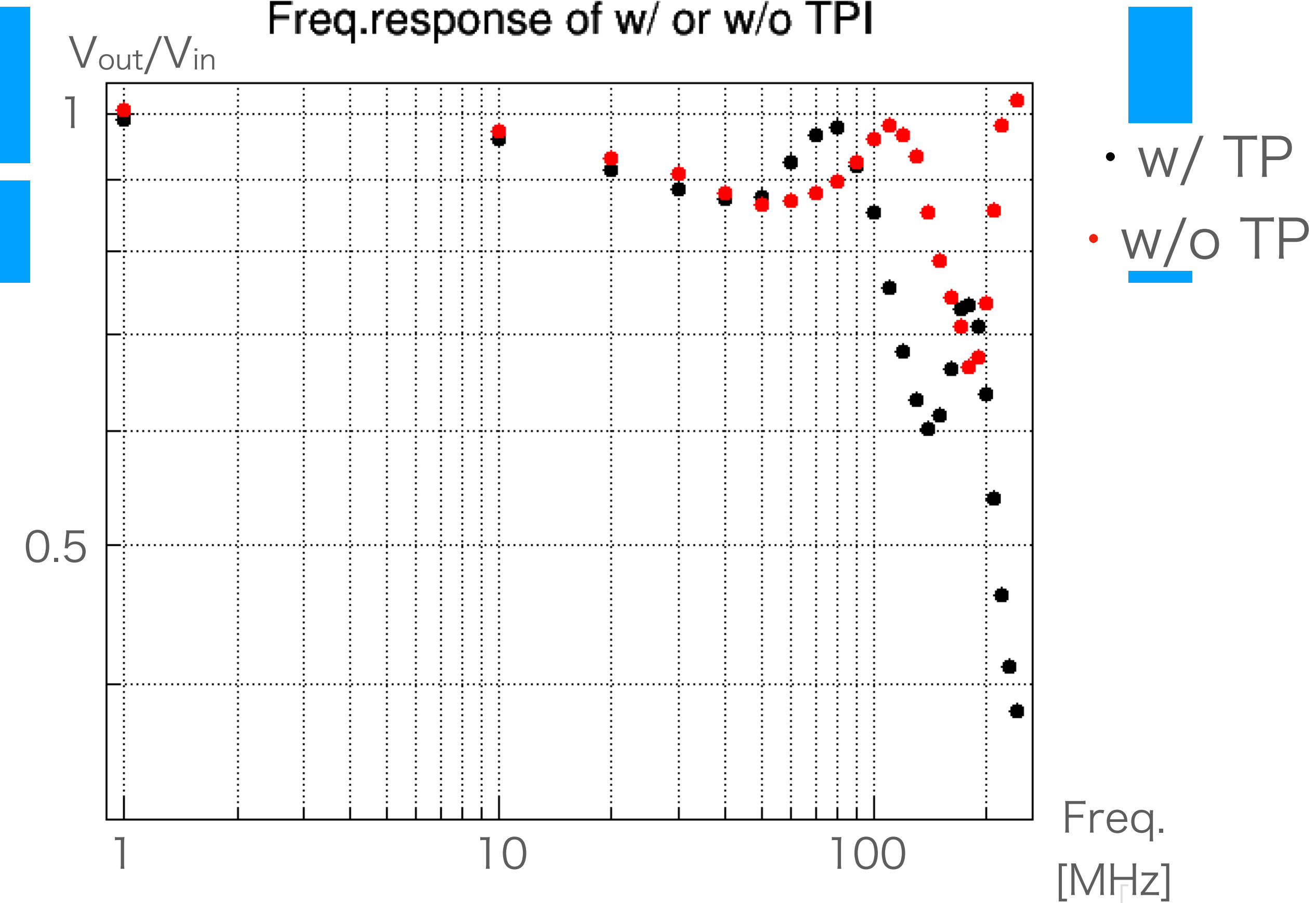Used sine wave,
measured V_{pp} ,
calculated ratio



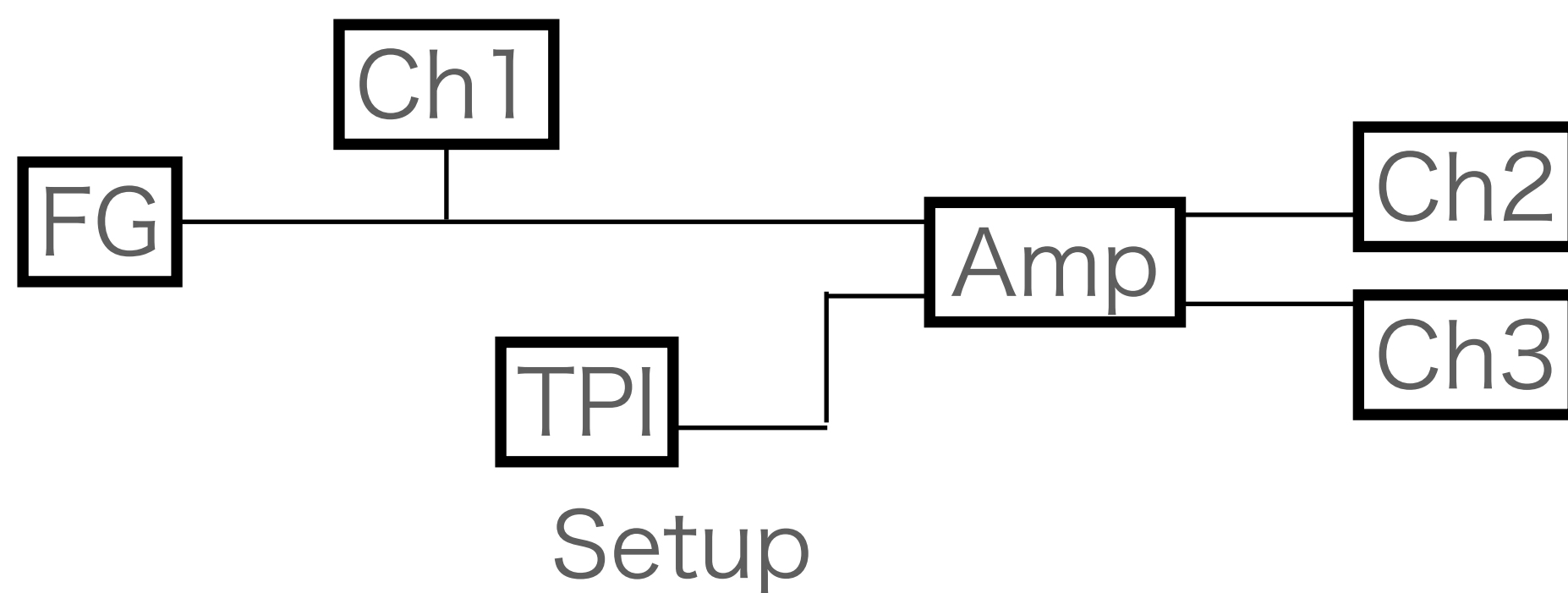
- Ratio was about 1 up to 10MHz
- Both plots are consistent up to 50 MHz



Design of a new board

Differences from previous one

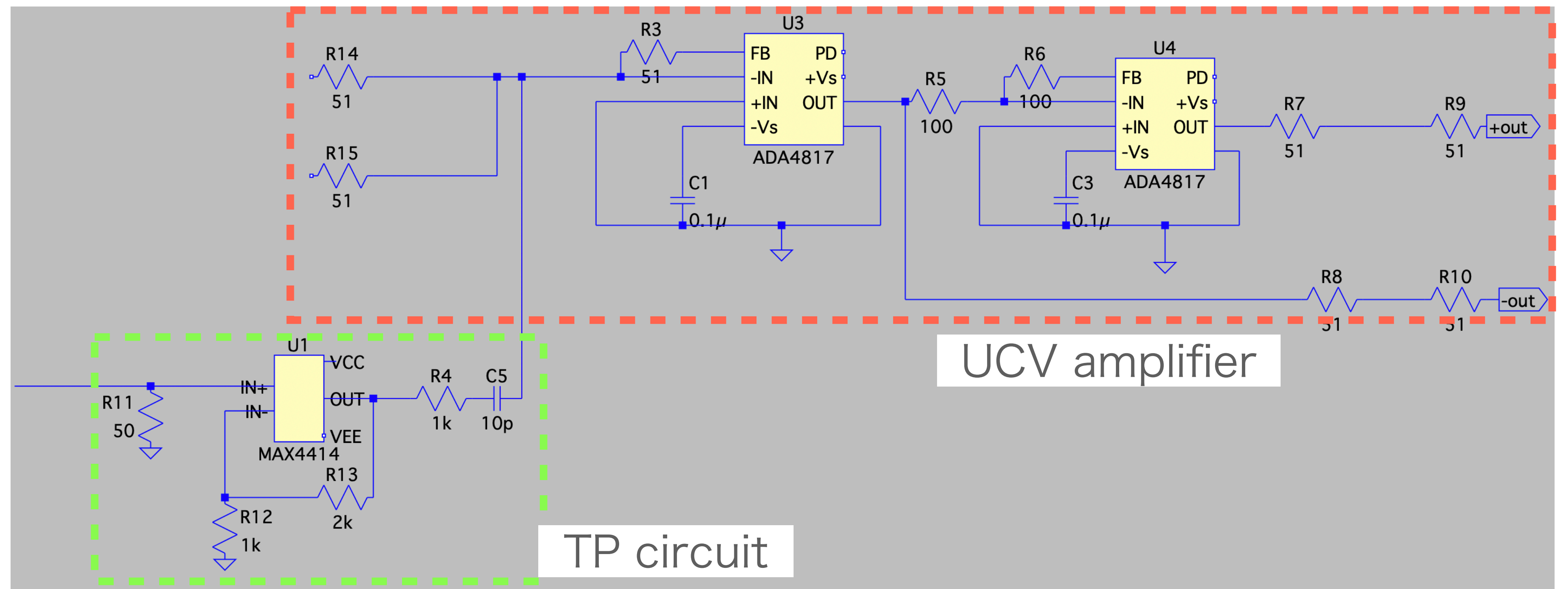
- The new design adds TP circuit to the original board




TP circuit and UCV amplifier are on the same board

Conclusion and Current status

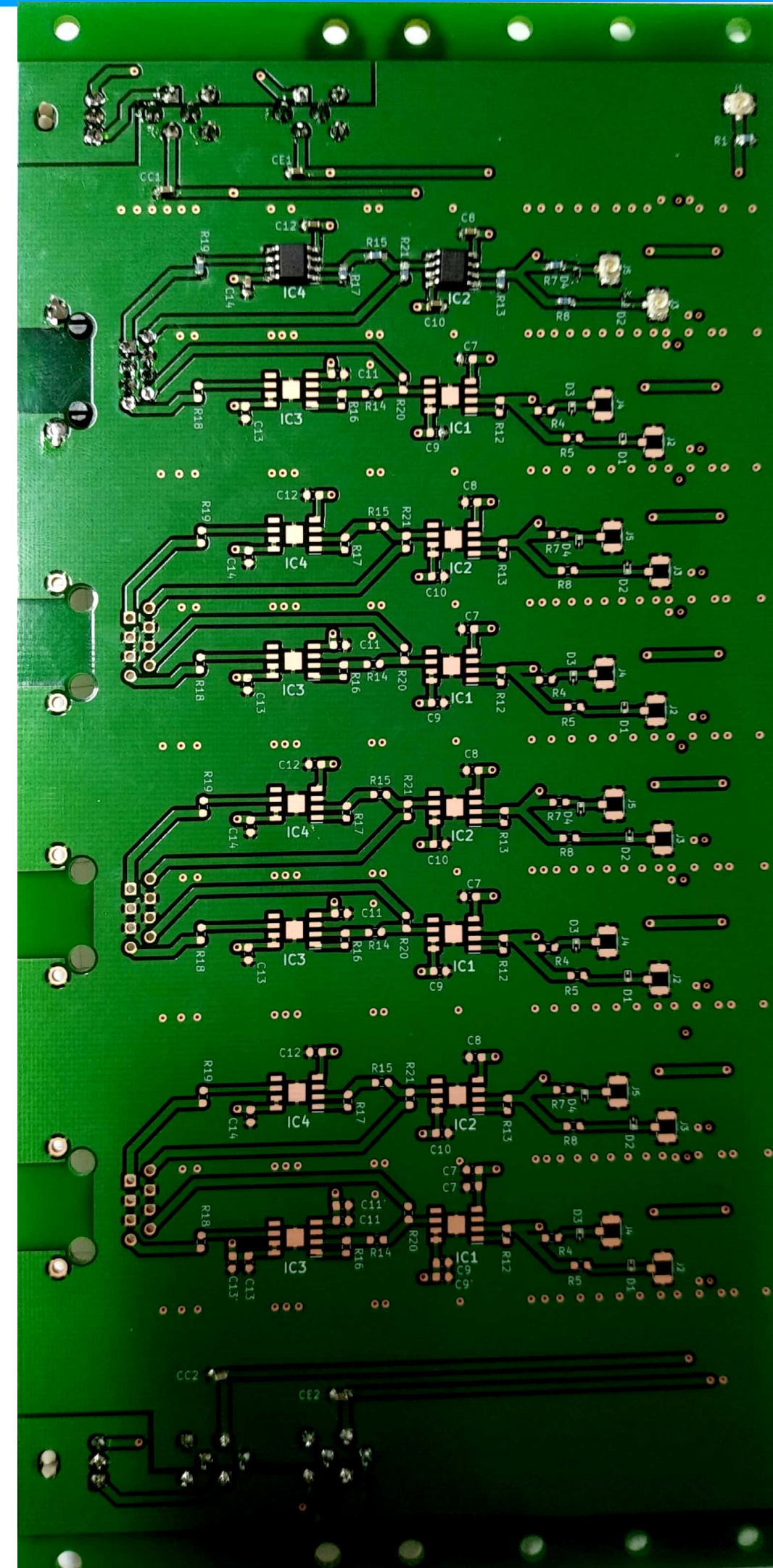- I developed TP circuit, did operation check -> meet demands
- I designed new board of UCV amplifier, ordered it
- Next -> operation check of new board



Back

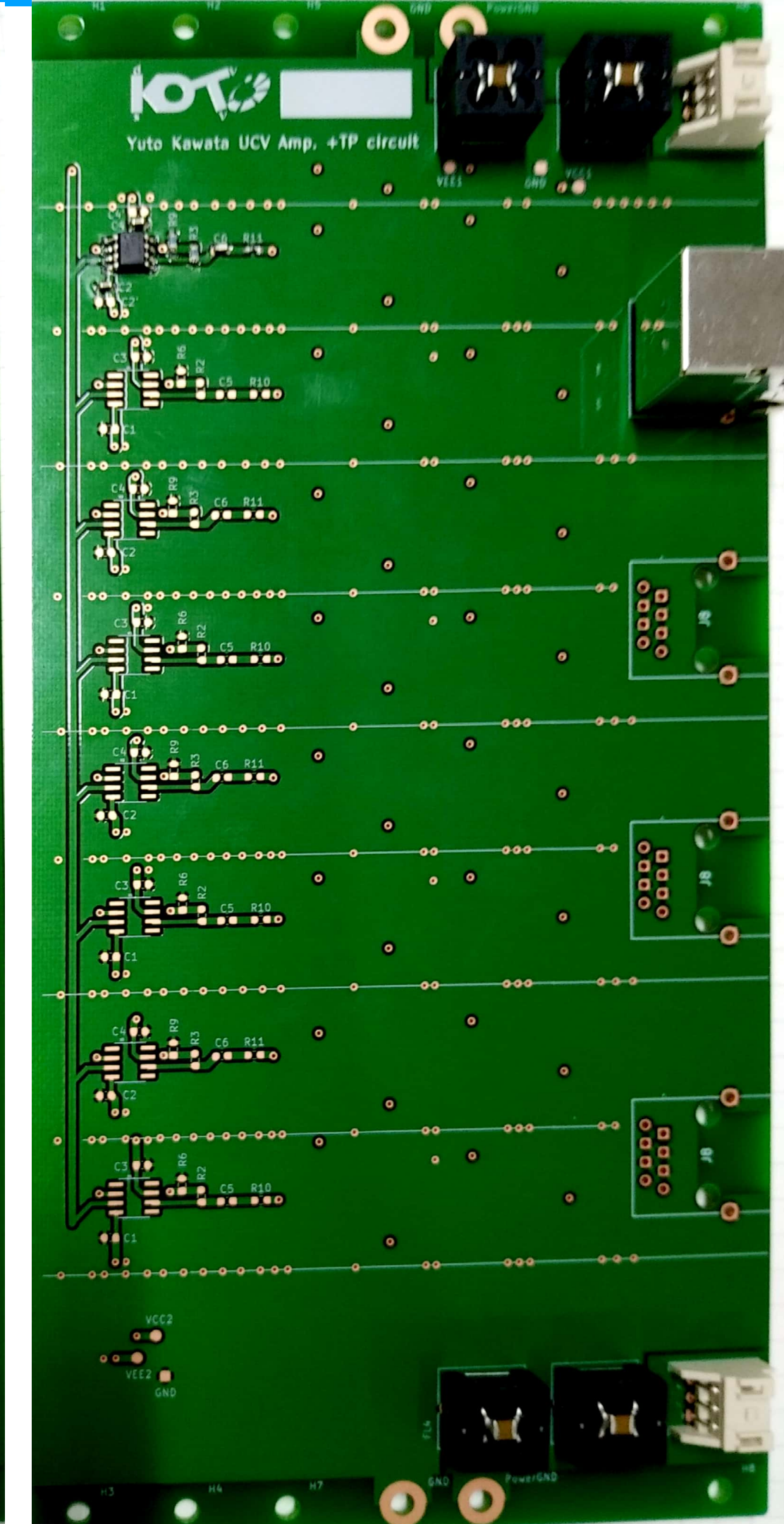


Front

Backup

Design

Op amp that is used in the UCV amplifier

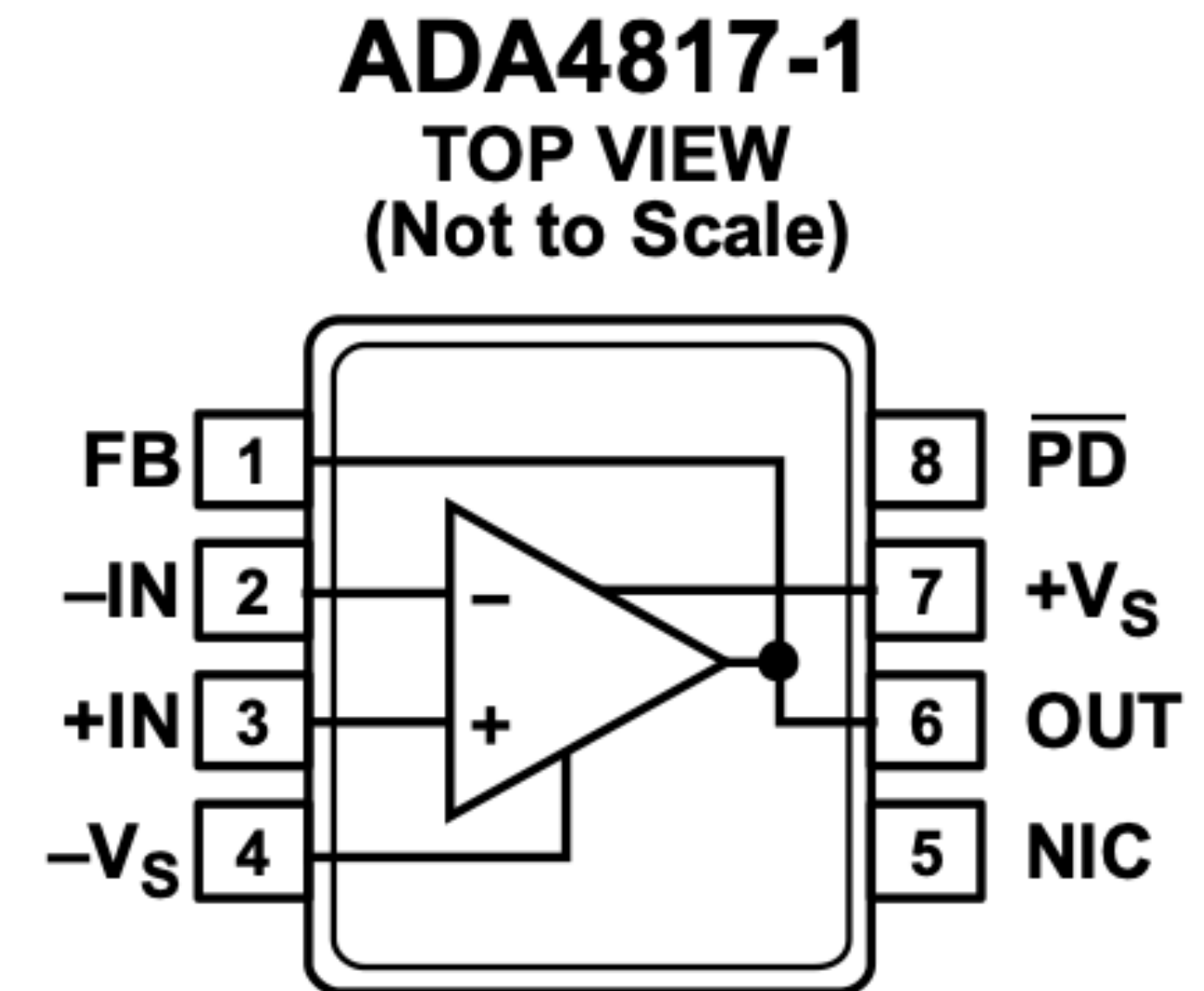- ADA4817-1ARDZ
- https://www.mouser.jp/datasheet/2/609/ADA4817_1_4817_2-2955817.pdf



NOTES

1. NIC = NO INTERNAL CONNECTION.


07756-002

Design

Op amp that is used in the TPI circuit

- MAX4414
- https://datasheets.maximintegrated.com/jp/ds/MAX4414-MAX4419_jp.pdf



TOP VIEW

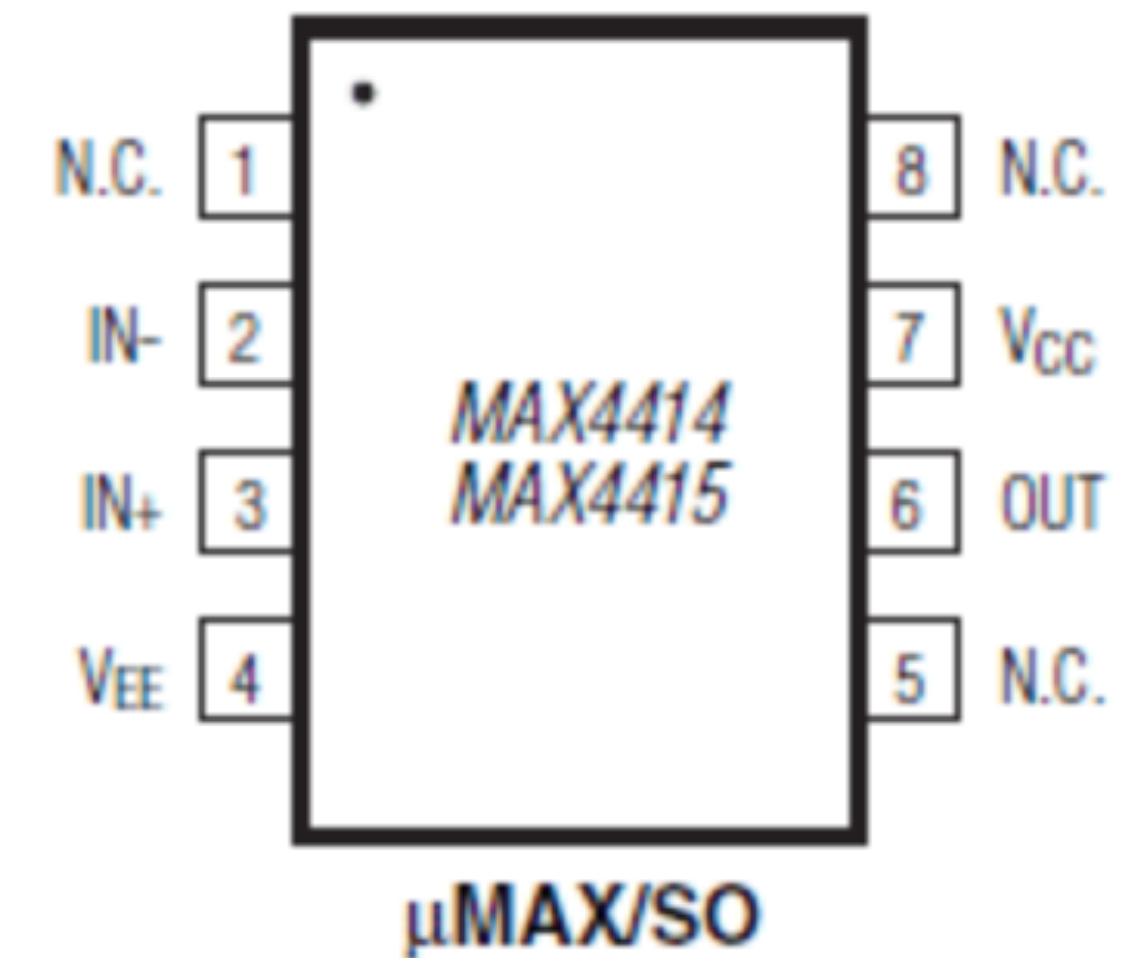

Test Pulse (TP) circuit

Role & Motivation

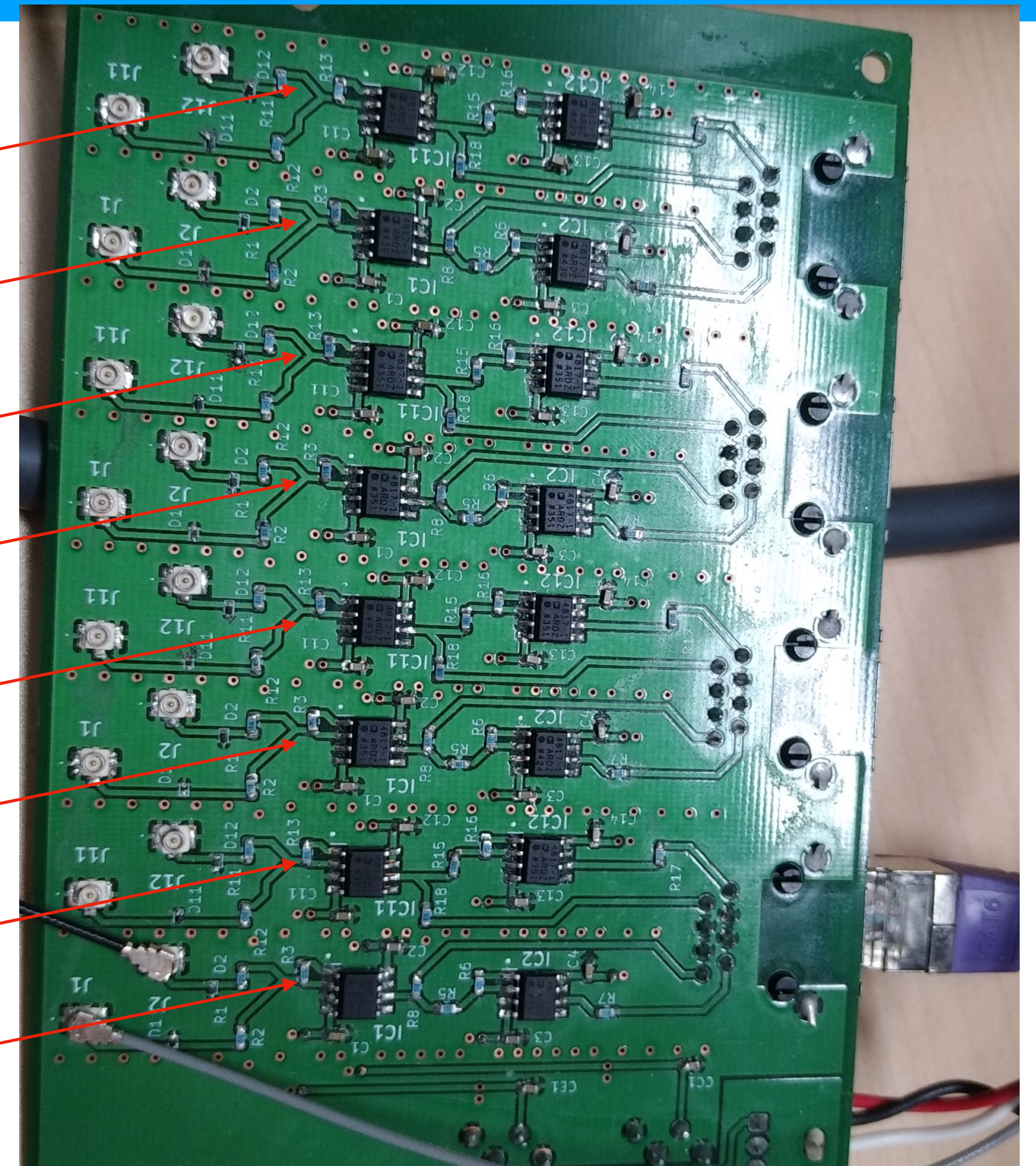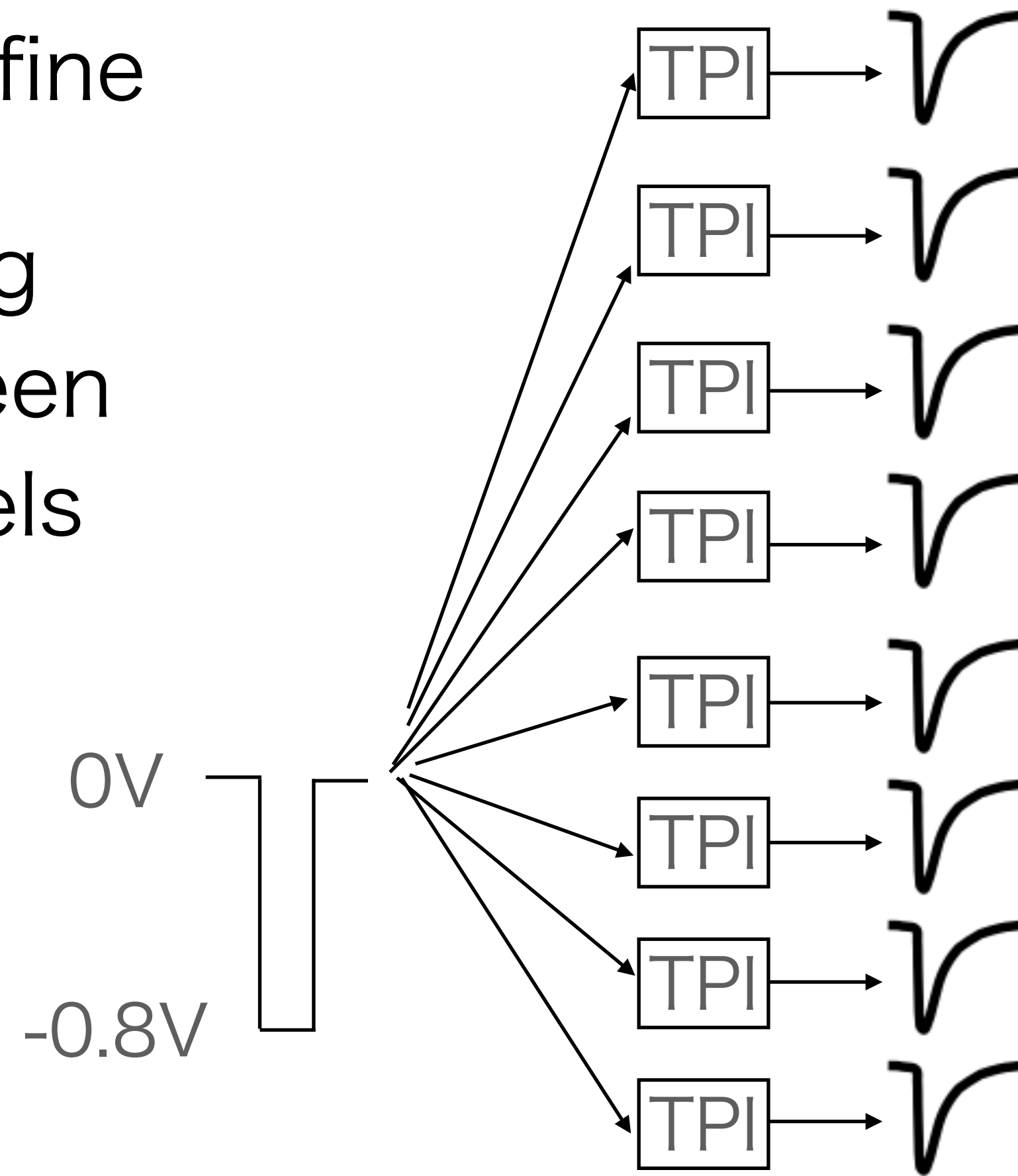
- Check the UCV amplifier works fine
- Check the timing variations between amplifier channels



Test Pulse (TP) circuit


Circuit diagram

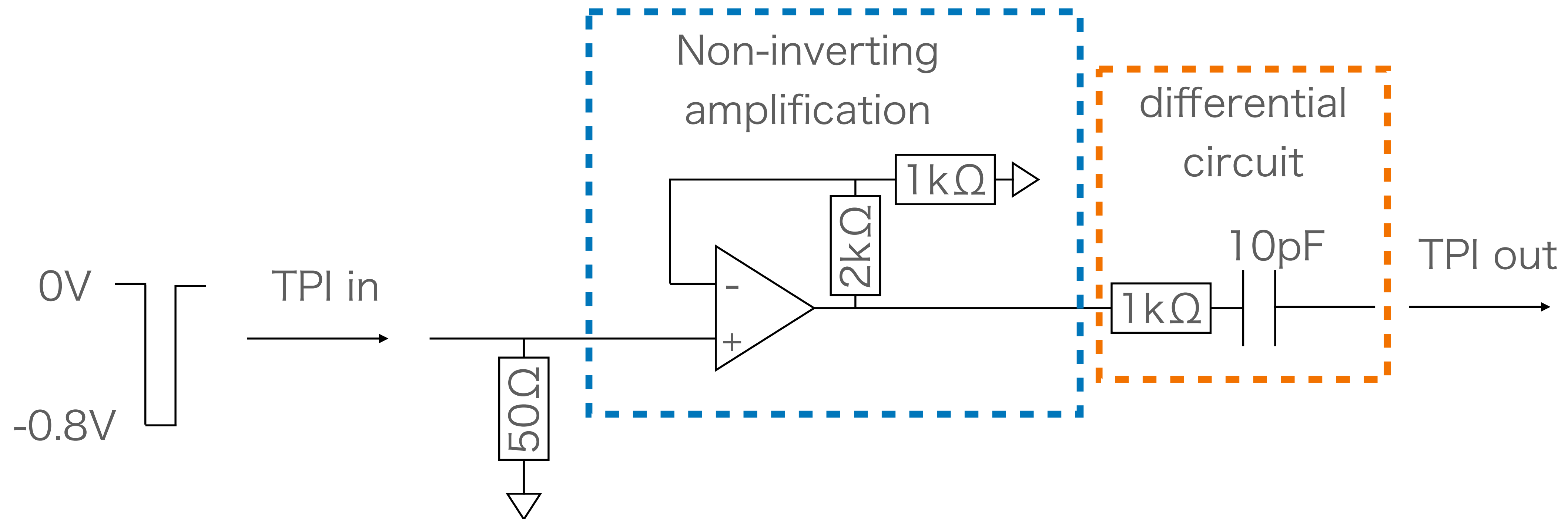- Op amp of TP circuit has the same performance as in the MPPC test pulse circuit
- Op amp has high enough frequency response(400 MHz for -3dB bandwidth)



Simulation

Result(check 1)

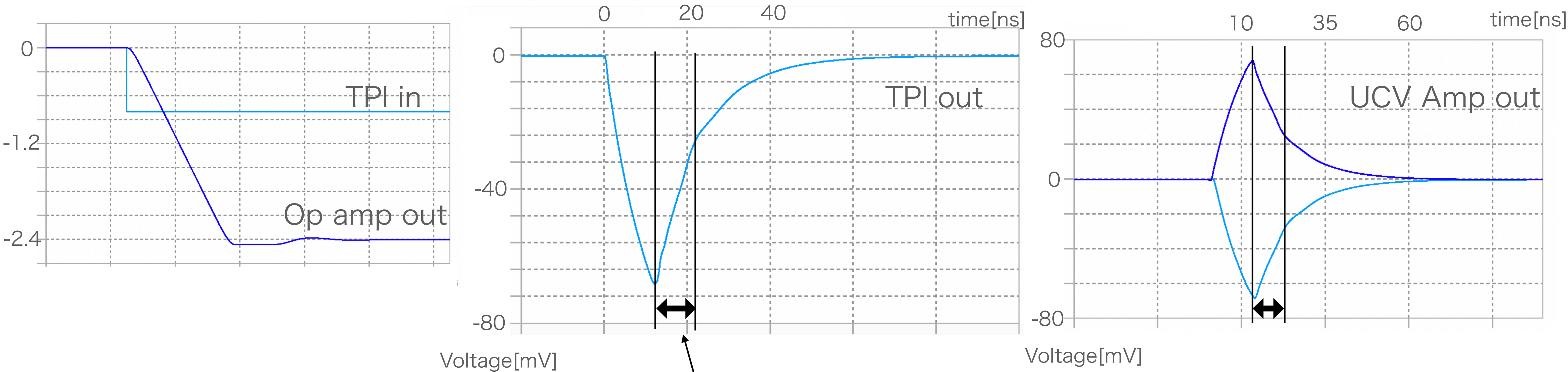


Time taken for wave height to become $1/e$

- time constant : $1 \text{ k}\Omega \times 10 \text{ pF} = 10 \text{ ns}$
- Measured time : 10 ns (TPI out), 9.5 ns (UCV Amp out)

Simulation



Result(check2)

- $V_{out} = |(+out)| + |(-out)|$
- Input-output ratio was about 1 up to 20 MHz

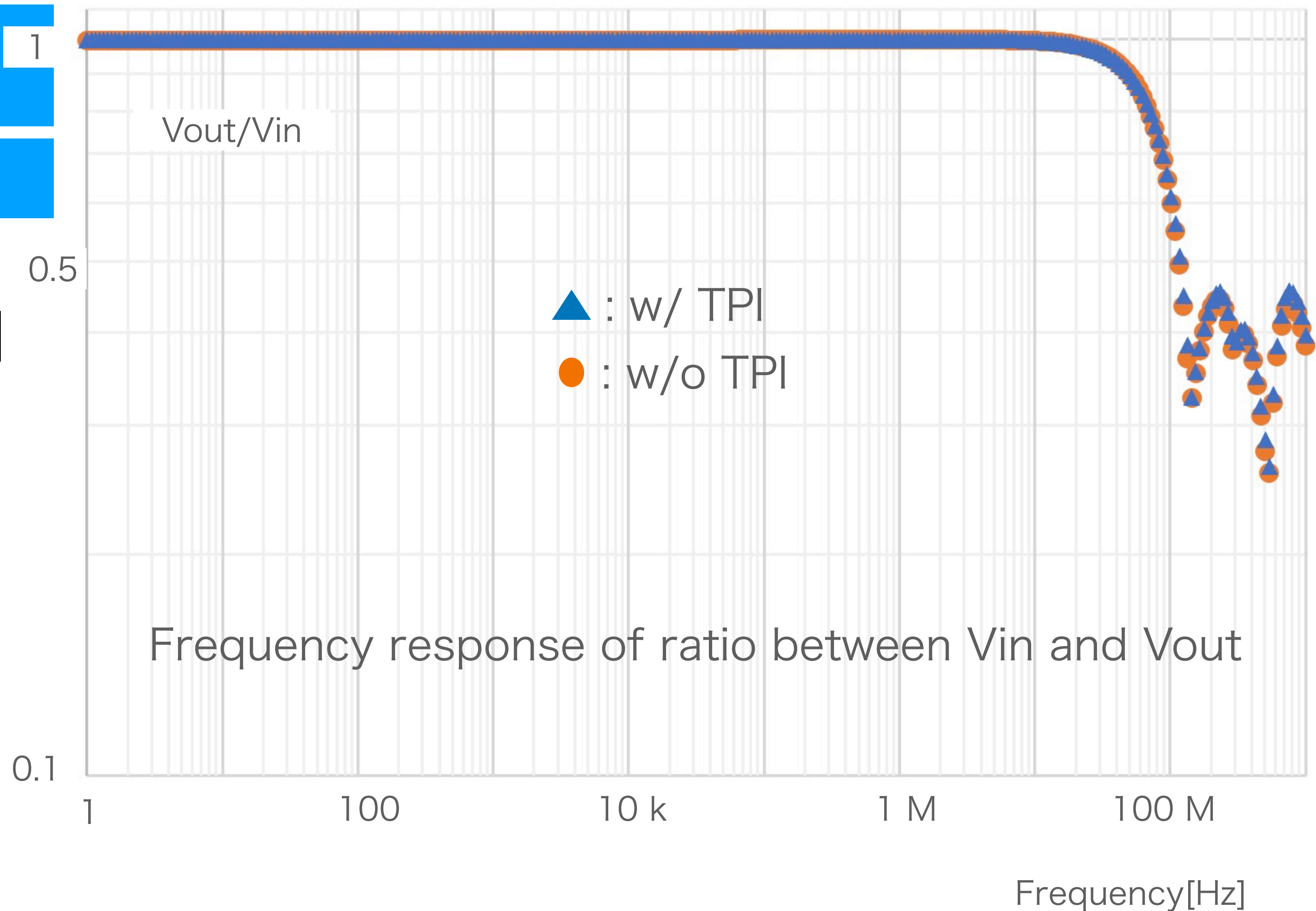


Operation check

Output waveform

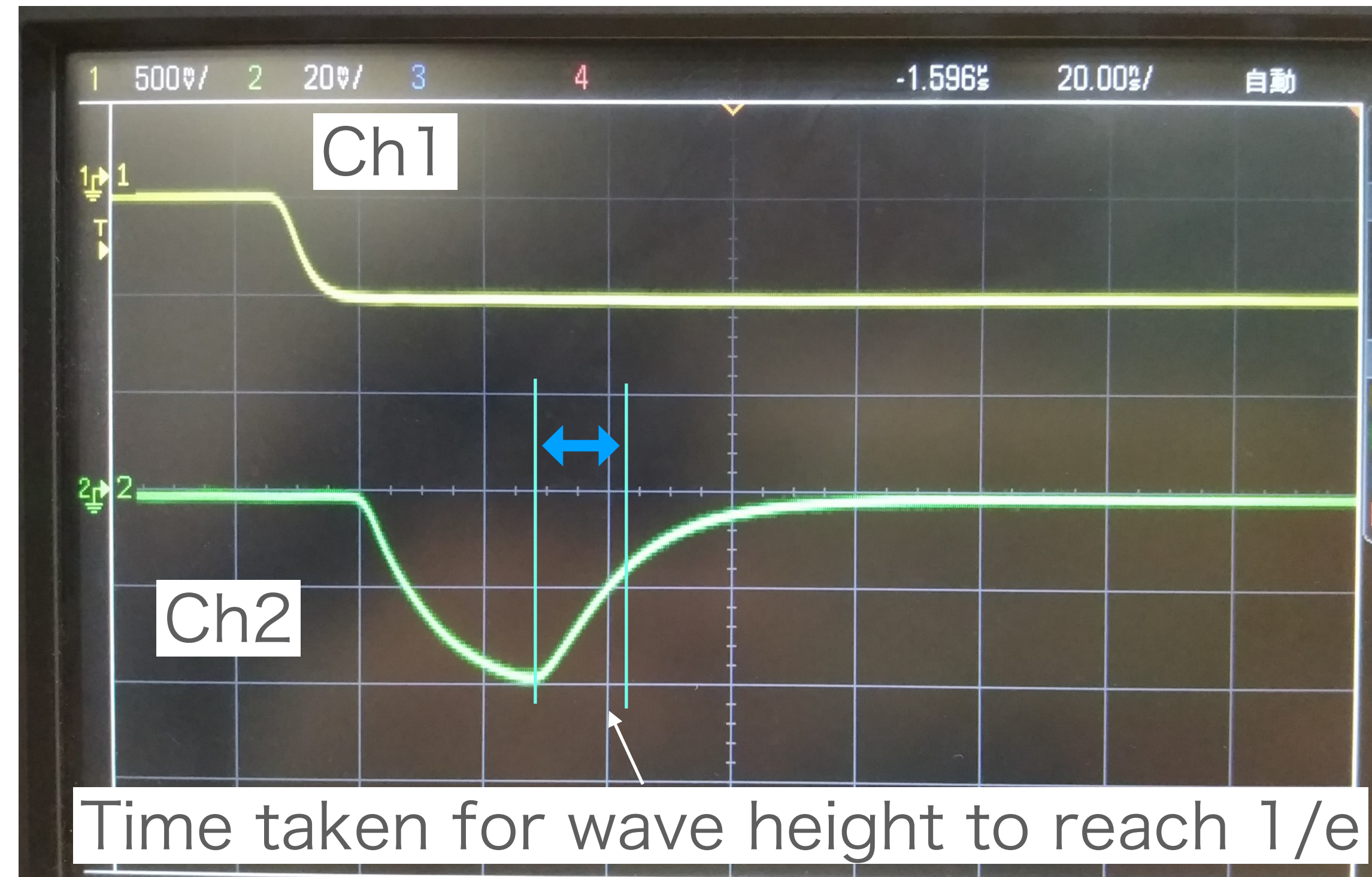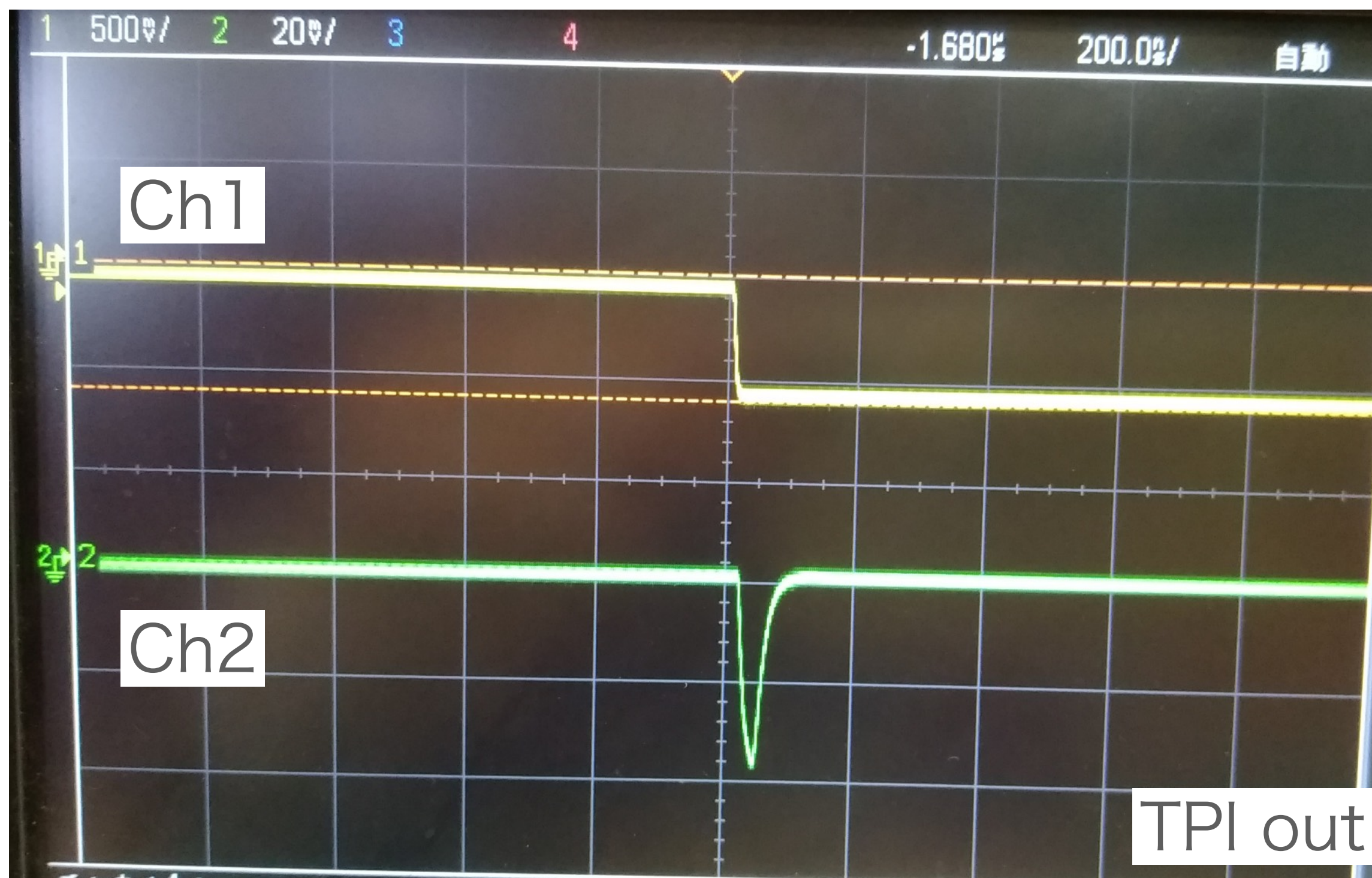

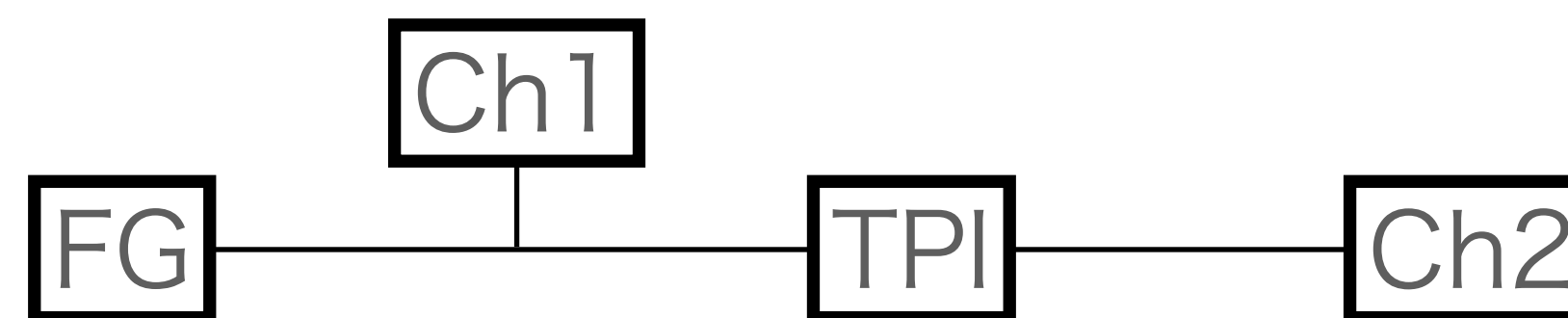- Time constant(calculated) : 10 ns
- Measured time : 15 ns



Problem

Voltage[V]	2.500
Current[A]	0.0030

Setting of DC power supply



- When I touched the pattern, supply voltage dropped. It didn't occur with insulators
- Voltage drop was recovered by cycling power
- Masking the trace with Kapton tape prevented the voltage drop
- Cycling the DC power with remotely control can fix the problem if it occurs in the beam time

Standby
↓
Signal in
↓
Touch
↓
Output off->on

State	-V Output	+V Output
Standby	2.504V, 0.0016A	2.490V, 0.0008A
Signal in	2.504V, 0.0020A	2.490V, 0.0005A
Touch	0.588V, 0.0032A	1.775V, 0.0023A
Output off->on	2.504V, 0.0020A	2.490V, 0.0005A

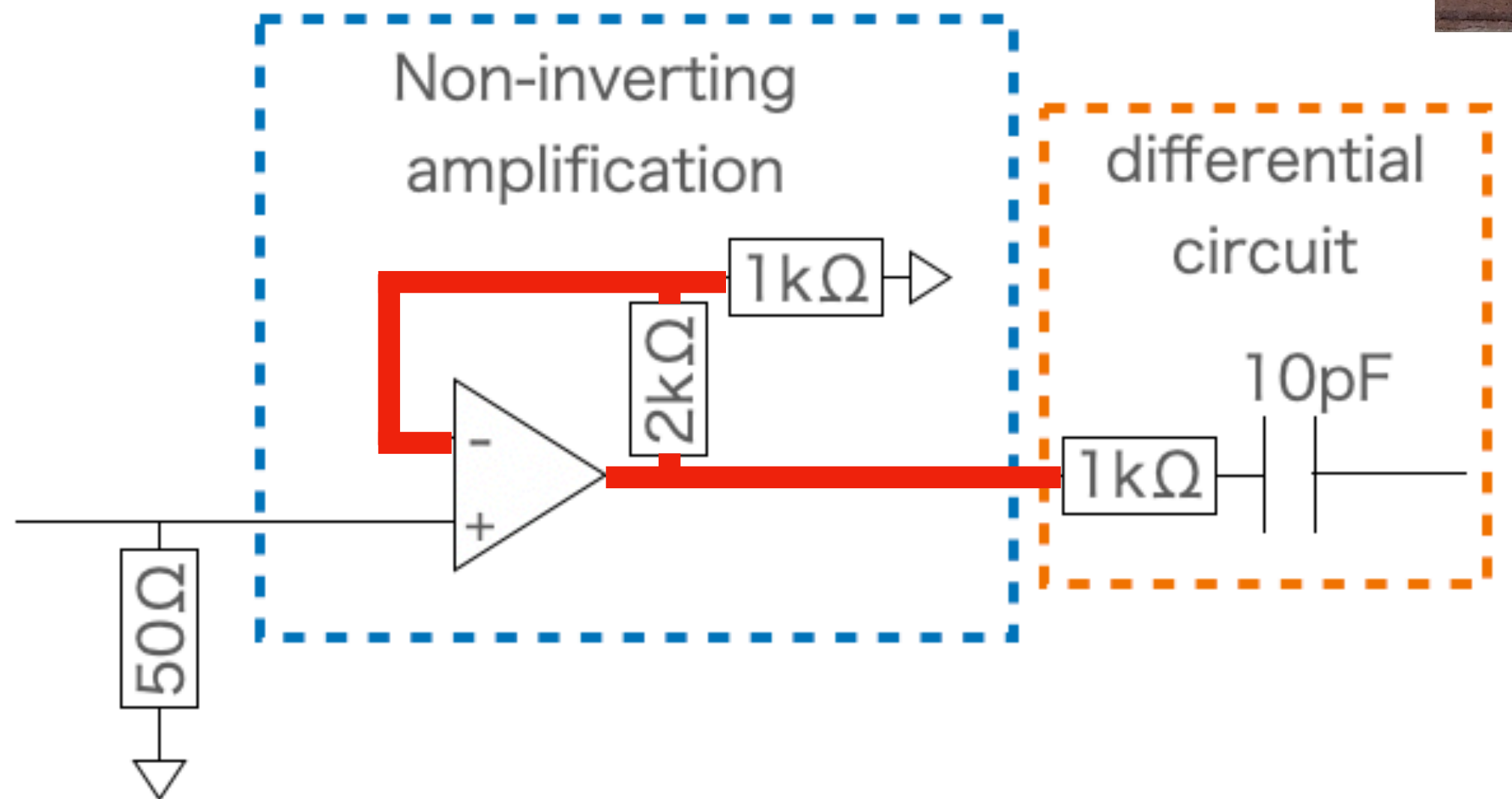
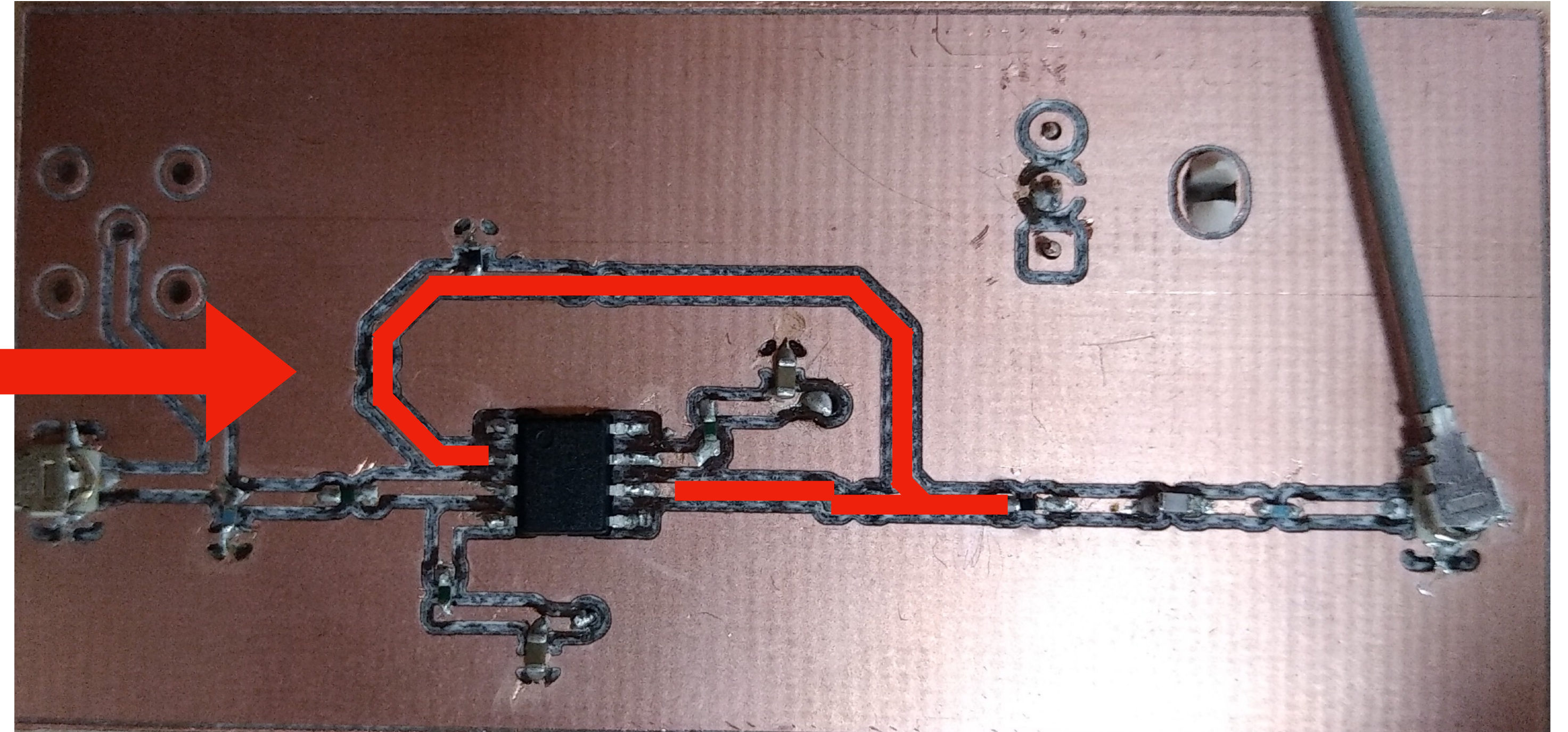
Problem

- Red line ;
voltage drop occurred when
we touched



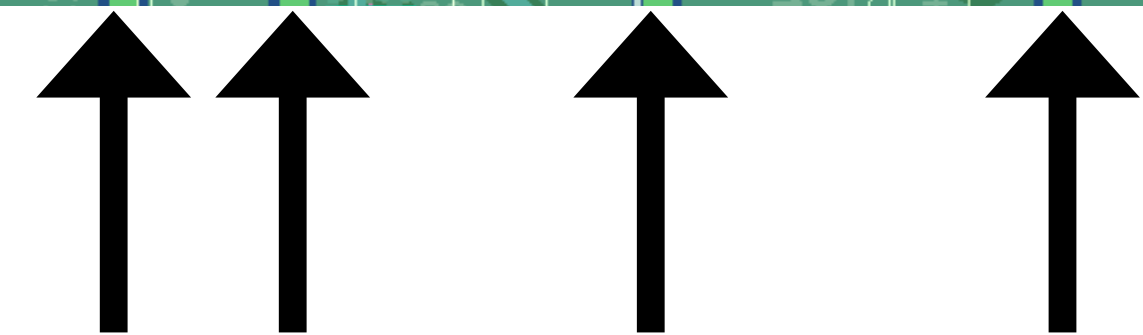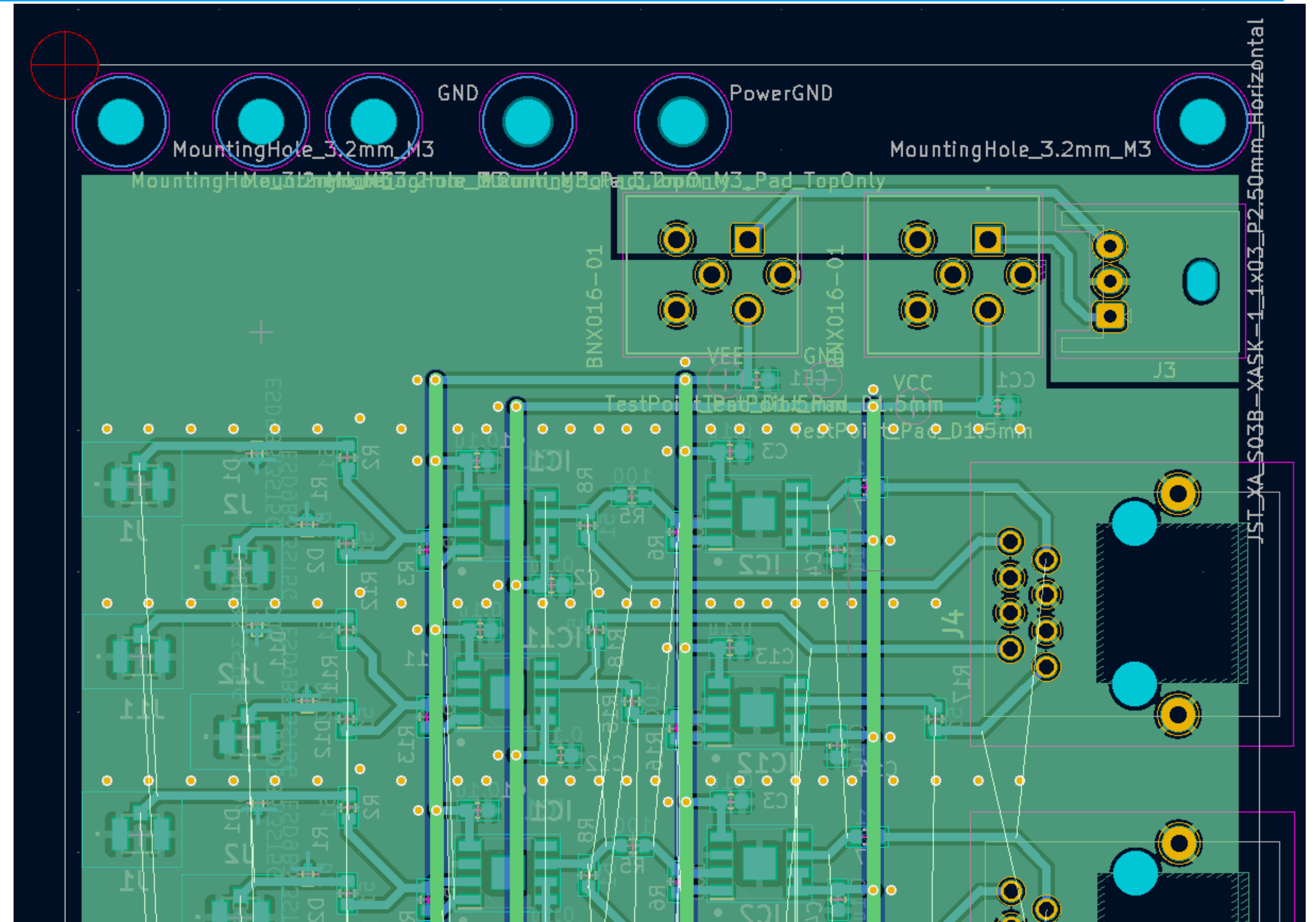Problem of current amp

- Amplifier far from power supply input was unstable
-> wider trace may help





Power supply trace

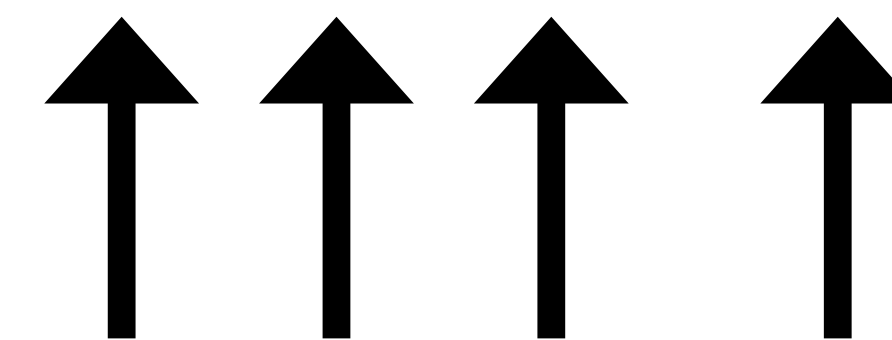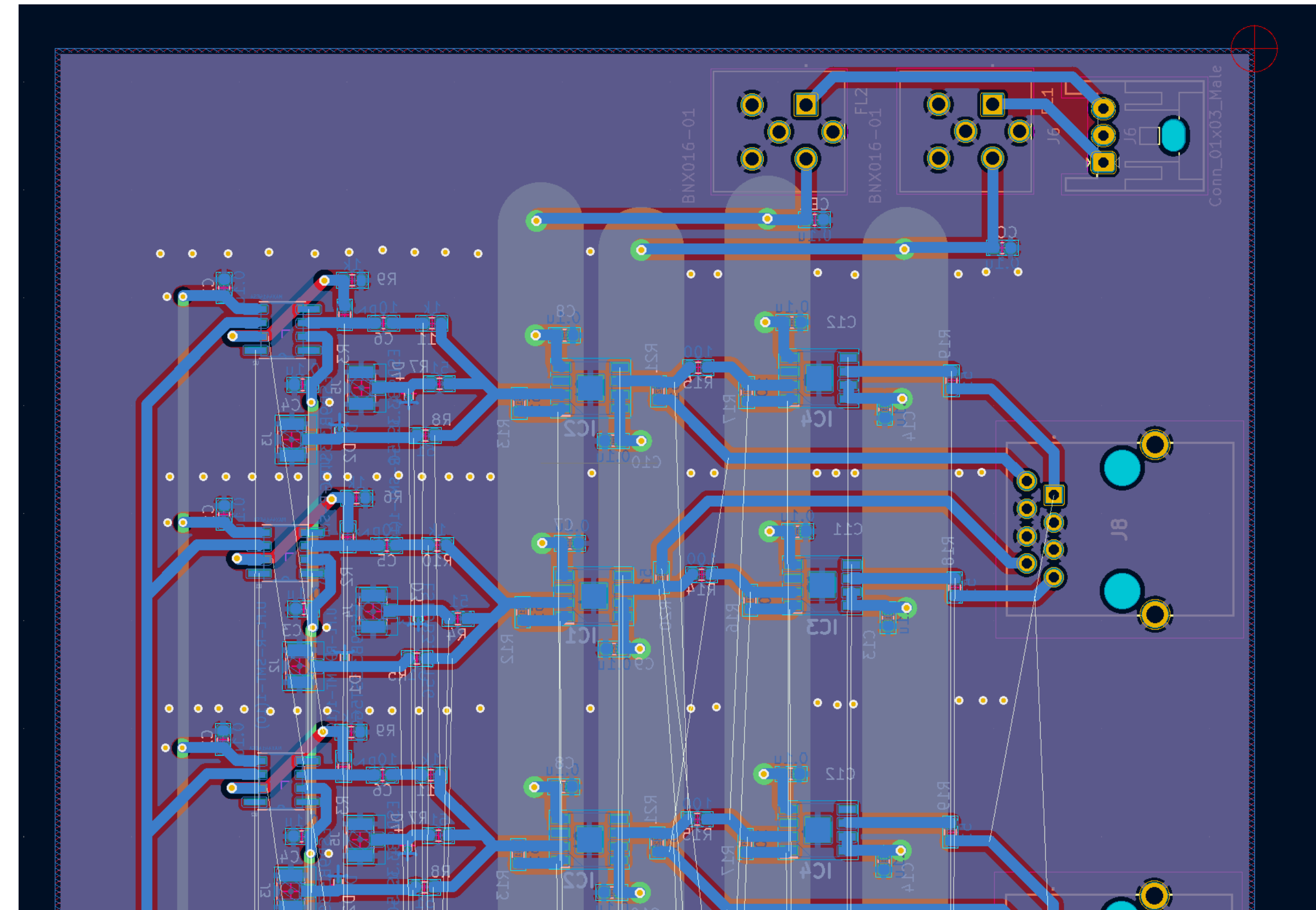Problem of current amp

Design of new board

- Amp + TP circuit
- Wider power supply trace



Power supply trace